

DIGITAL LOGIC(H)

Chapter 4 part2: Standard Components


2024 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.
Please do not repost it on other platforms without permission from the instructor.

Today's Agenda

- Recap
- Context
 - Decoder
 - Multiplexer
 - Encoder
- Reading: Textbook, Chapter 4.9-4.11
 - Next Lecture we continue to chapter 5
 - Arithmetic Logic will be taught later

Recap

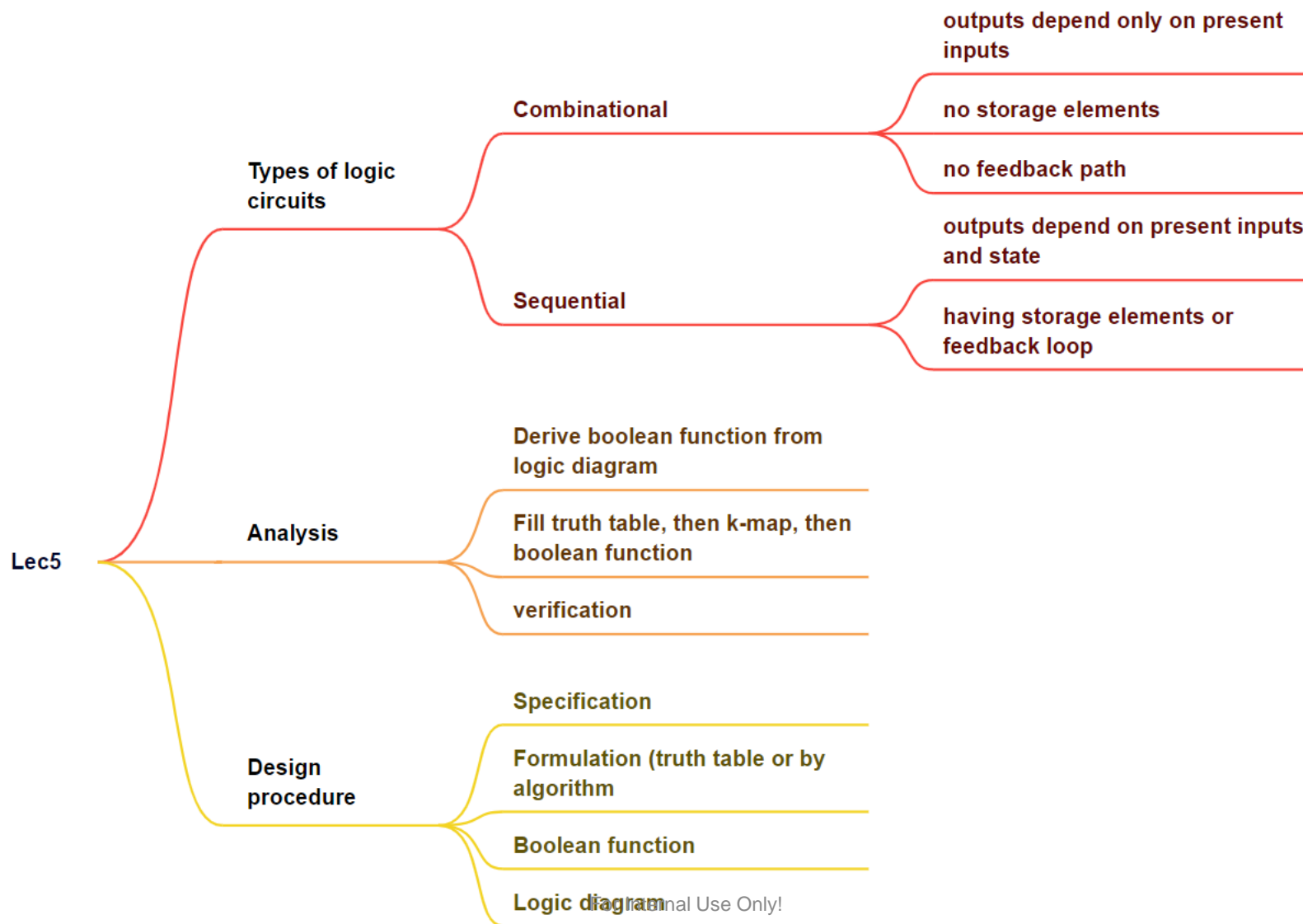

Outline

- **Decoder**
- Multiplexer
- Encoder


One-hot Representation

- Represent a set of N elements with N bits
- Exactly one bit is set

Binary	One-hot
000	00000001
001	00000010
010	00000100
011	00001000
100	00010000
101	00100000
110	01000000
111	10000000

Decoder

- A decoder is a combinational circuit that converts binary information from n input lines to m (maximum of 2^n) unique output lines
 - n -to- m -line decoder
- A binary one-hot decoder converts a symbol from binary code to a one-hot code
 - Output variables are mutually exclusive because only one output can be equal to 1 at any time (the 1-minterm)
- Example
 - binary input a to one-hot output b
 - $b[i] = 1$ if $a = i$ or $b = 1 \ll a$
 - a stands for position of 1 in b

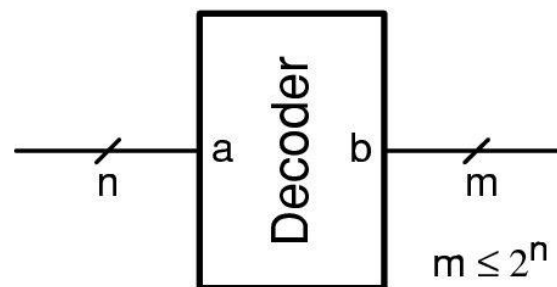

1-to-2-Line Decoder

- Step1: Specification
- Step2: Formulation

x	D ₁	D ₀
0	0	1
1	1	0


- Step3: Optimization

$$D_0 = x'$$

$$D_1 = x$$

↙ minterms
↘

- Step4: Logic Diagram

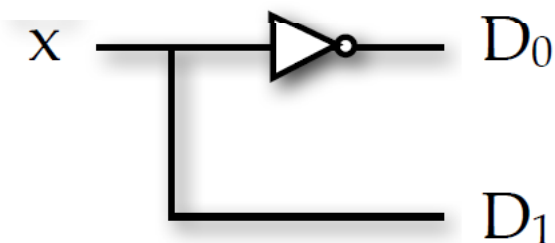

2-to-4-Line Decoder

Step 1,2


a_1	a_0	b_3	b_2	b_1	b_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Step 3

$$\begin{aligned} b_3 &= a_1 a_0 \\ b_2 &= a_1 a_0' \\ b_1 &= a_1' a_0 \\ b_0 &= a_1' a_0' \end{aligned}$$



Step 4

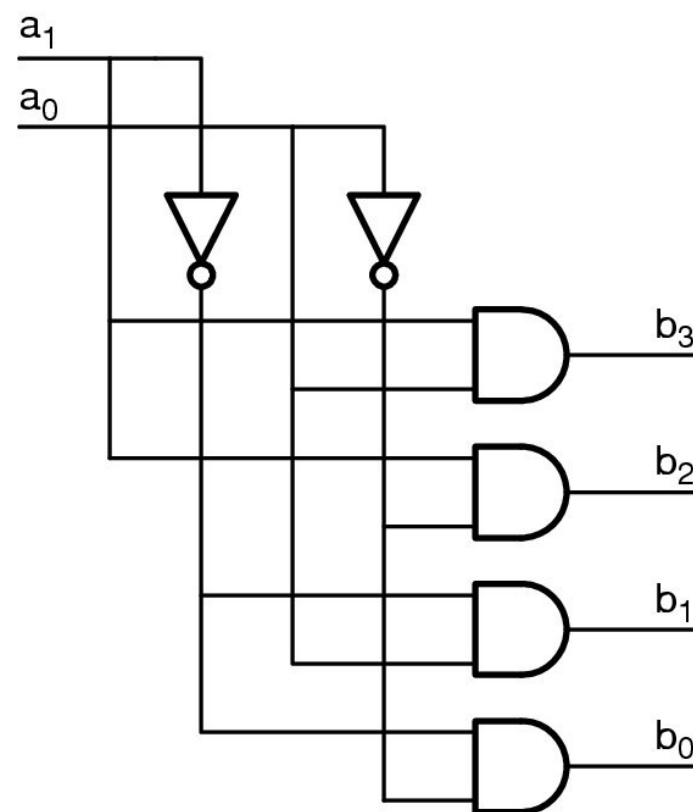


3-to-8-Line Decoder

- Each output of the decoder represents one of the eight minterms of the Boolean function

Step 1,2



Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Step 4

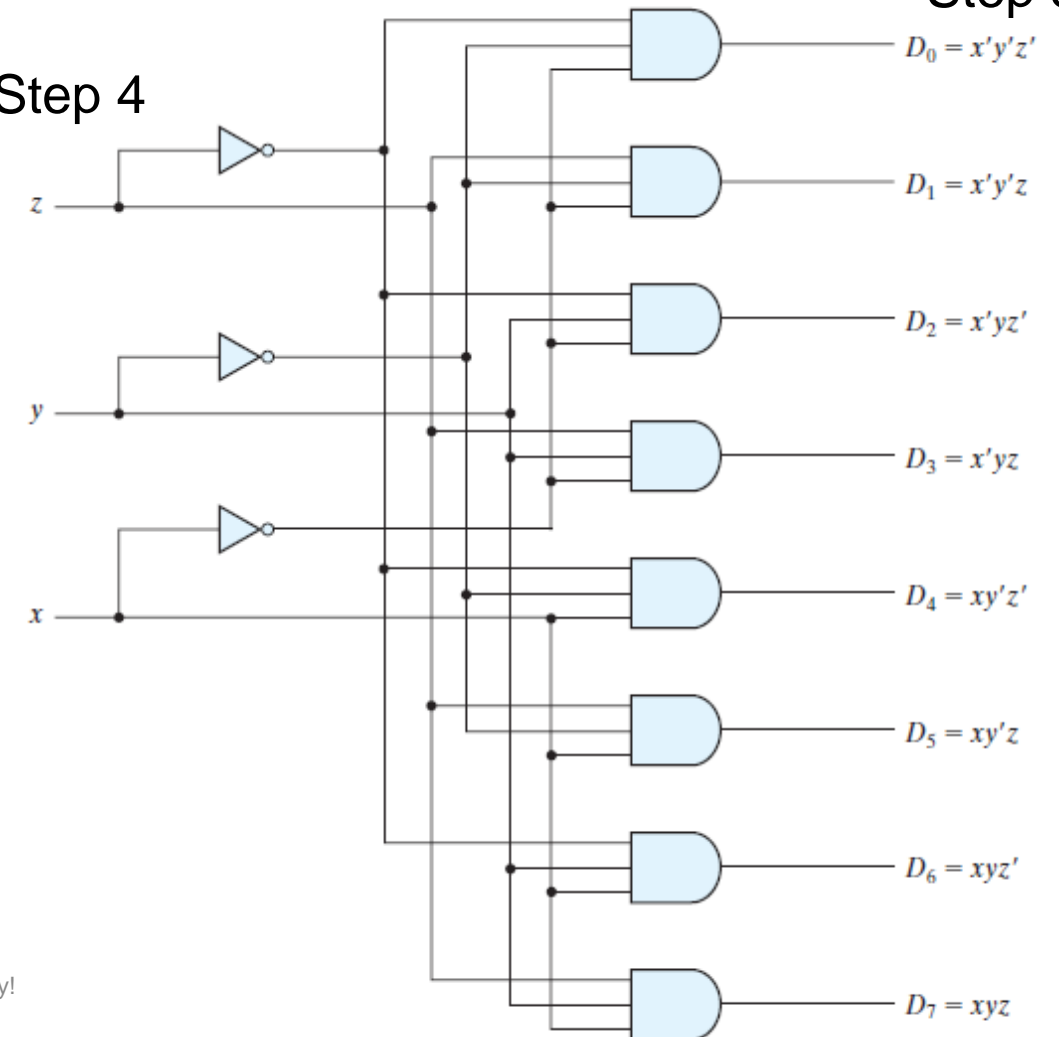

Graphic Symbol of Decoder

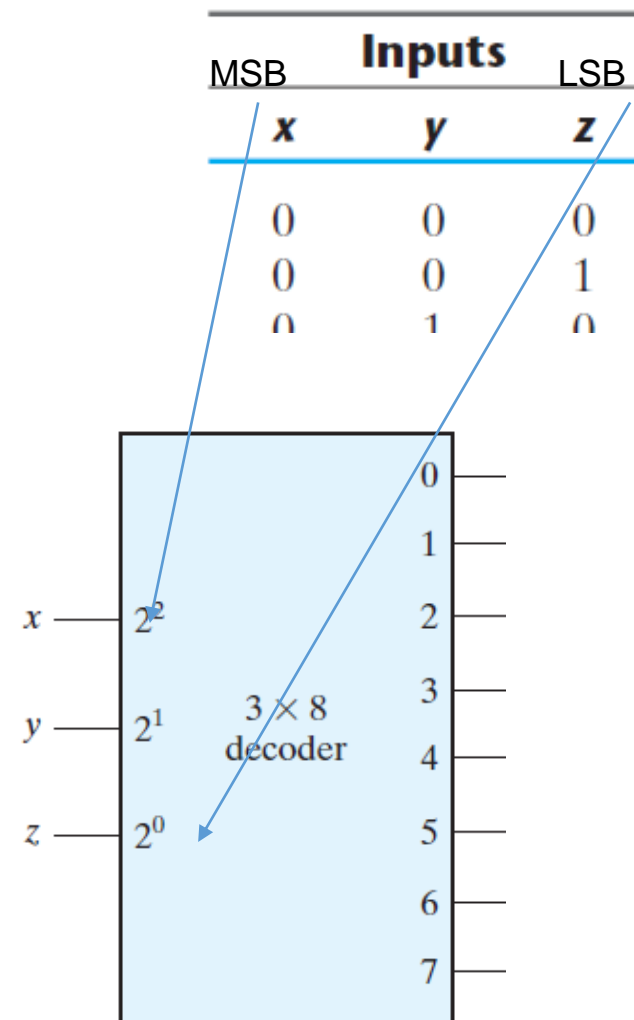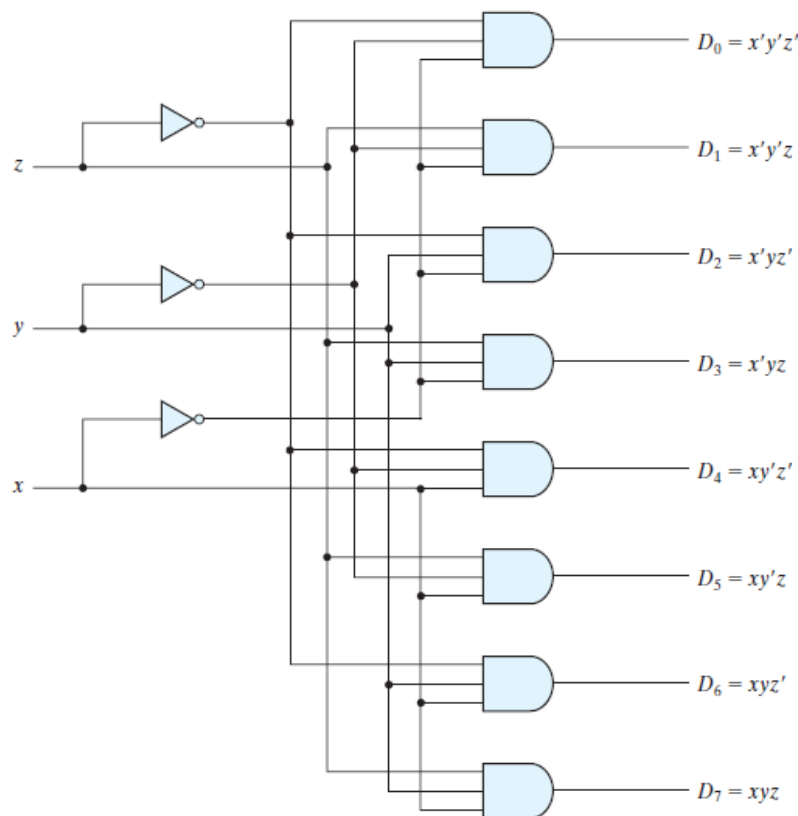- We can use graphic symbol/block diagram
 - You must clearly denoting the input and output within decoder's box



Main Usages of Decoders

- Minterm generator:
 - Generate the 2^n (or fewer) minterms of n input variables. For example: a 3-8 line decoder
- Data demultiplexing:
 - A decoder with enable input can function as a demultiplexer – a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
- Display decoding:
 - Decoders are used in display systems to select a specific output line based on the input code and drive the corresponding segment of the display.
- Address decoding:
 - Identify a memory cell, disk sector, or other memory or storage device, to ensure one device can communicate with the processor at one time.

Decoder for logic implementation


Example1

- Decoder can be used to implement the logic function by connecting the appropriate minterms to an OR gate.
 - Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder in conjunction with m external OR gates

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(x, y, z) = \sum(1, 2, 4, 7)$$

$$C(x, y, z) = \sum(3, 5, 6, 7)$$

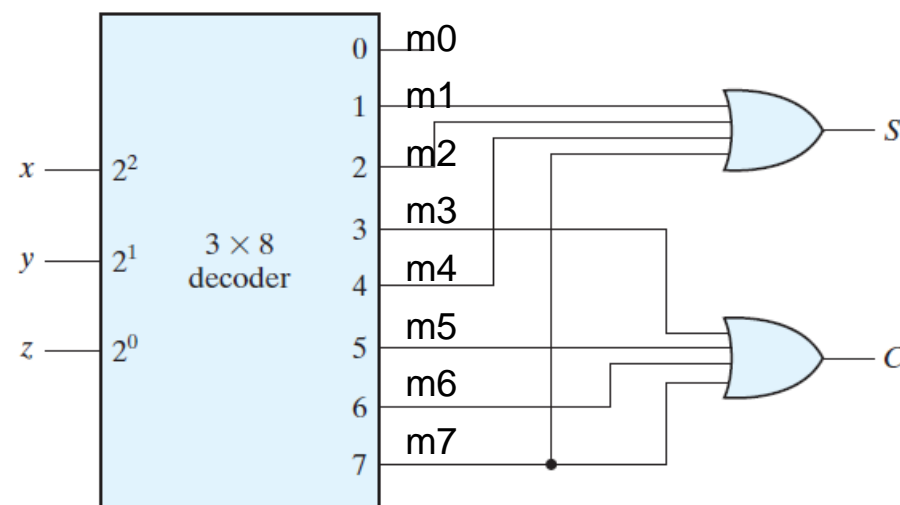


Decoder for logic implementation

Example2

- Exercise:
 - Implement $Y = A \text{ XNOR } B$ using a 2-to-4 line decoder and external OR gate, you need to clearly write down the input and output pins

$$\begin{aligned} Y &= A \text{ XNOR } B \\ &= (A \oplus B)' \\ &= A'B' + AB \\ &= \sum(0, 3) \end{aligned}$$

Connect output 0 and 3
to an OR gate

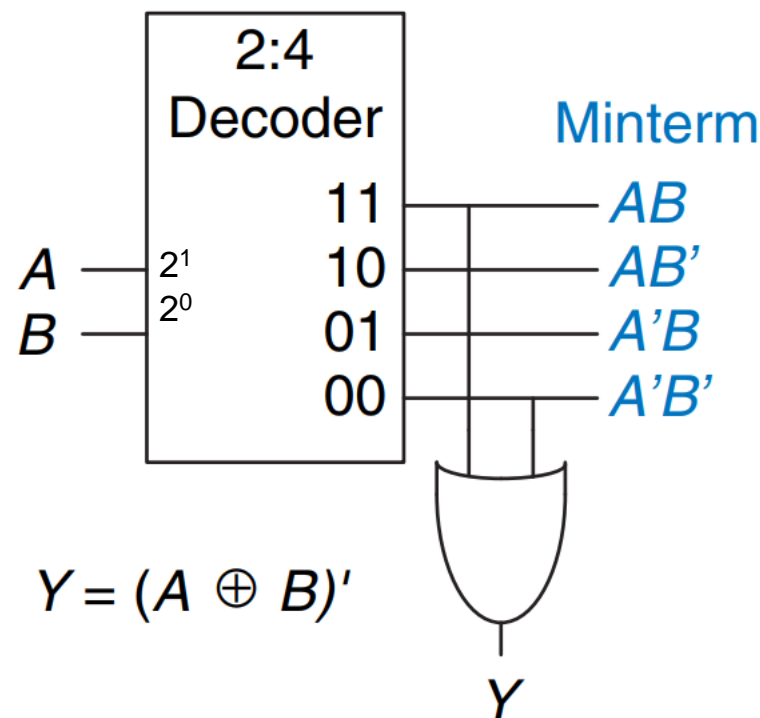


For Internal Use Only!

Manufacturer: Major Brands

Decoder for logic implementation

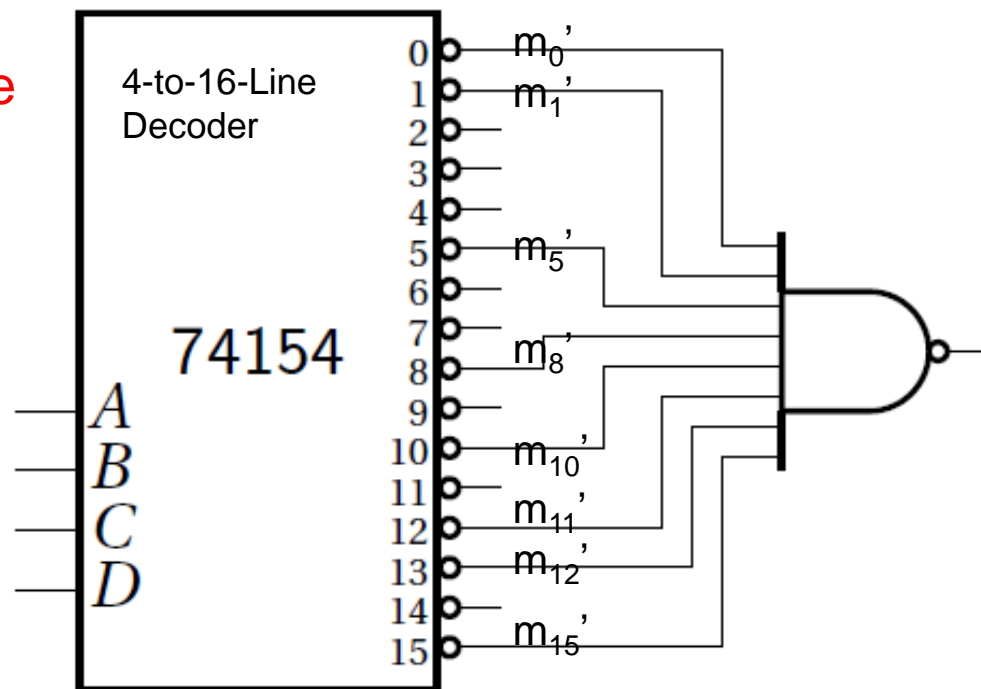
Example3

- Using 74154 for logic function implementation
 - 74154: a 4-to-16 line decoder
 - Characteristics: If $A = B = C = D = 0$ the output 0 of the decoder is **0** while all other outputs are 1. (**active low output**) → generate inverse of minterms
- Example:
 - $F(A,B,C,D) = \sum(0, 1, 5, 8, 10, 12, 13, 15)$.
 - $= [(m_0 + m_1 + m_5 + m_8 + m_{10} + m_{12} + m_{13} + m_{15})']'$
 - $= (m_0' \cdot m_1' \cdot m_5' \cdot m_8' \cdot m_{10}' \cdot m_{12}' \cdot m_{13}' \cdot m_{15}')$
 - thus a nand gate is used instead of an or gate



Enabling

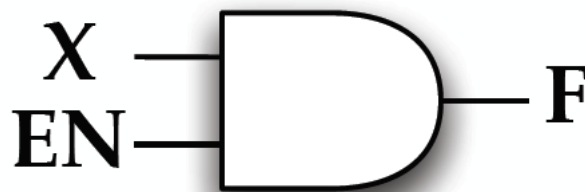- Enabling permits an input signal to pass through to an output.



- $F = EN \cdot X$


EN	X	F
0	0	0
0	1	0
1	0	0
1	1	1

Decoder with Enable Input

- Decoder with enable control (E)

Step1,2


	E	A ₀	C ₁	C ₀
Active High Enable	1	0	0	1
	1	1	1	0
Low → disabled	0	X	0	0

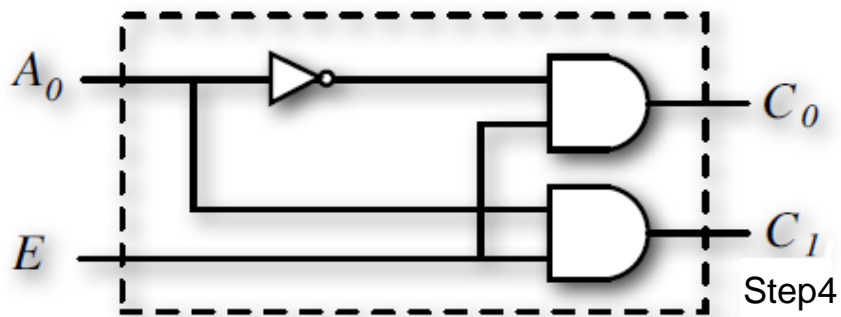

Step3

$$C_0 = EA_0'$$

$$C_1 = EA_0$$

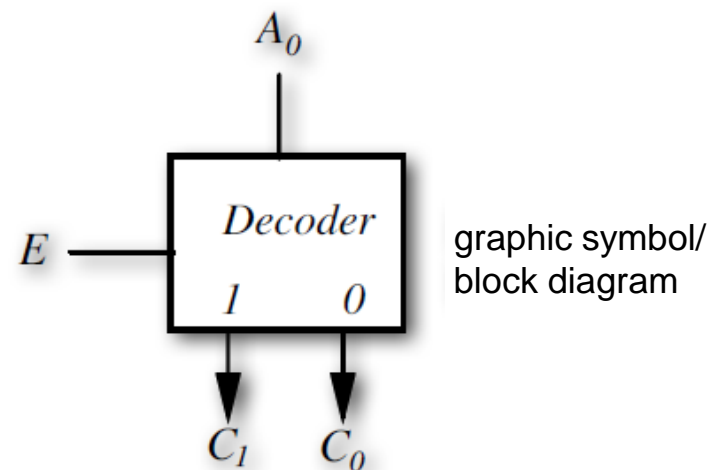


1-2 Line Decoder with Enable

Decoder with Active-Low Enable


- If constructed with NAND gates
 - decoder minterms in their complemented form (more economical)

	E	A	B	D_0	D_1	D_2	D_3
High \rightarrow disabled	1	X	X	1	1	1	1
Active Low Enable	0	0	0	0	1	1	1
	0	0	1	1	0	1	1
	0	1	0	1	1	0	1
	0	1	1	1	1	1	0

Output in complement form

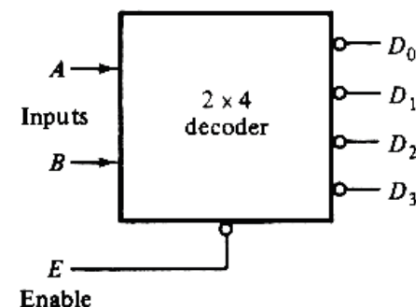

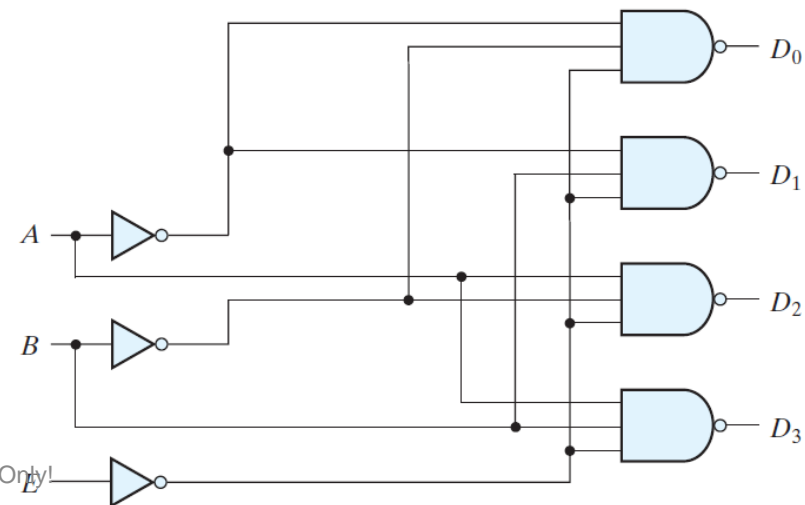
$$\begin{aligned} D_0 &= (E'A'B')' \\ D_1 &= (E'A'B)' \\ D_2 &= (E'AB')' \\ D_3 &= (E'AB)' \end{aligned}$$



For Internal Use Only

Decoder Expansion

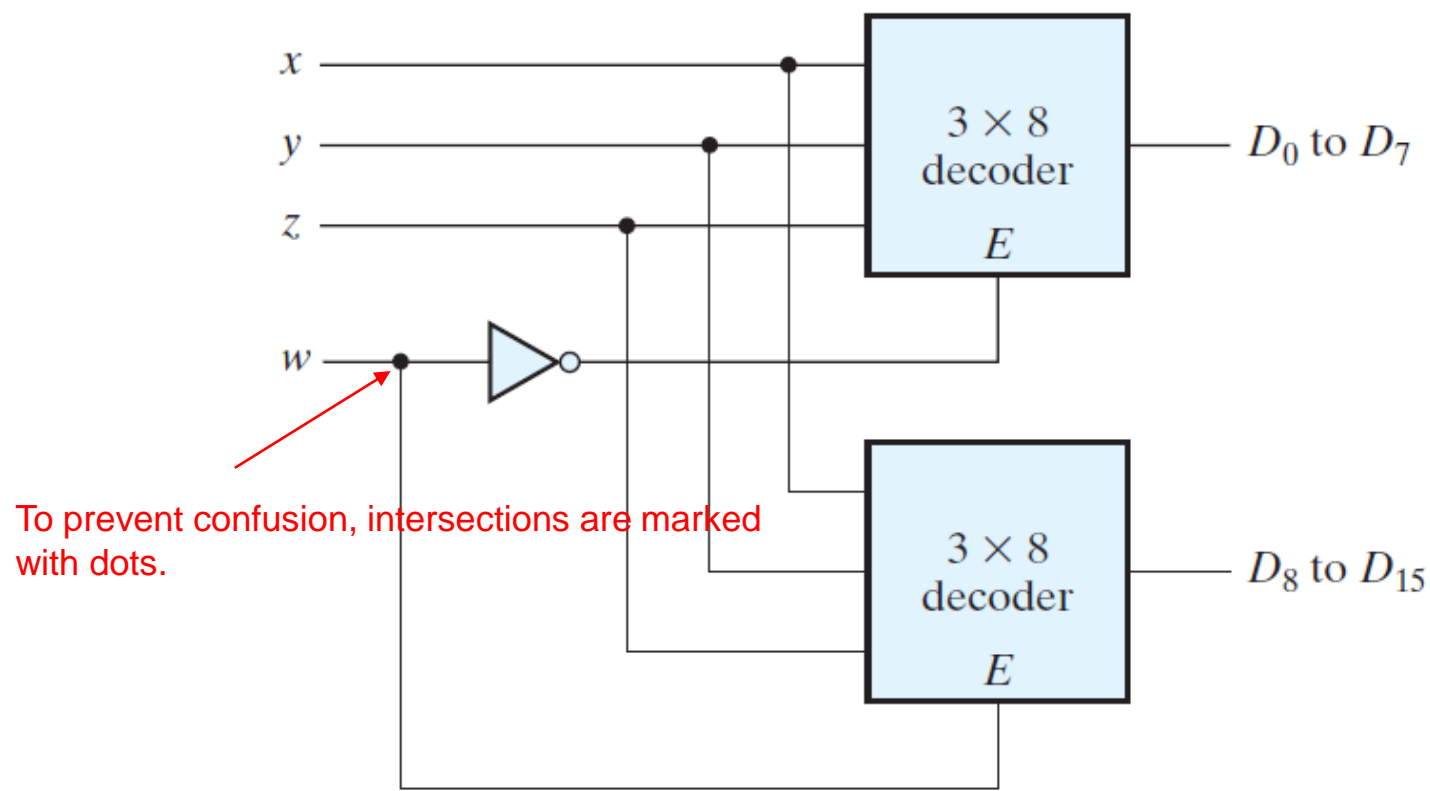- Larger decoders can be implemented with smaller decoders
- Question, is this decoder's enable active high or low?





A 4-to-16-line decoder from two 3-to-8-line decoders

Other Decoders

- BCD-to-7-Segment Display Decoder
 - input (ABCD), output (abcdefg)(MSB to LSB)
 - ABCD:0000~1001(0~9)

BCD Input				7-Segment Display						
A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	0	0	1	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	0	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
All other inputs				0	0	0	0	0	0	0

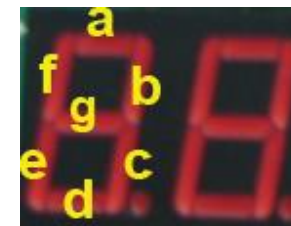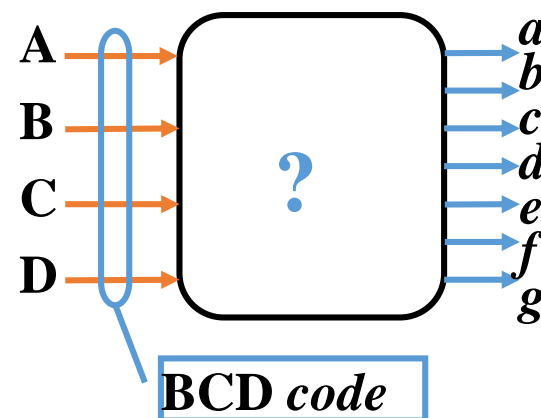


$$\begin{aligned}
 a &= A'C + A'BD + B'C'D' + A'B'C' \\
 b &= A'B' + A'C'D' + A'CD + AB'C' \\
 c &= A'B + A'D + B'C'D' + AB'C' \\
 d &= A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D \\
 e &= A'CD' + B'C'D' \\
 f &= A'BC' + A'C'D' + A'BD' + AB'C' \\
 g &= A'CD' + A'B'C + A'BC' + AB'C'
 \end{aligned}$$

Outline



- Decoder
- **Multiplexer**
- Encoder

Multiplexers (MUX)

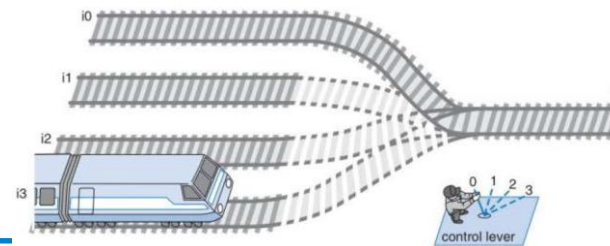

- A Multiplexer selects (usually by n select lines) binary information from one of many (usually 2^n) input lines and directs it to a single output line.

2:1 multiplexer

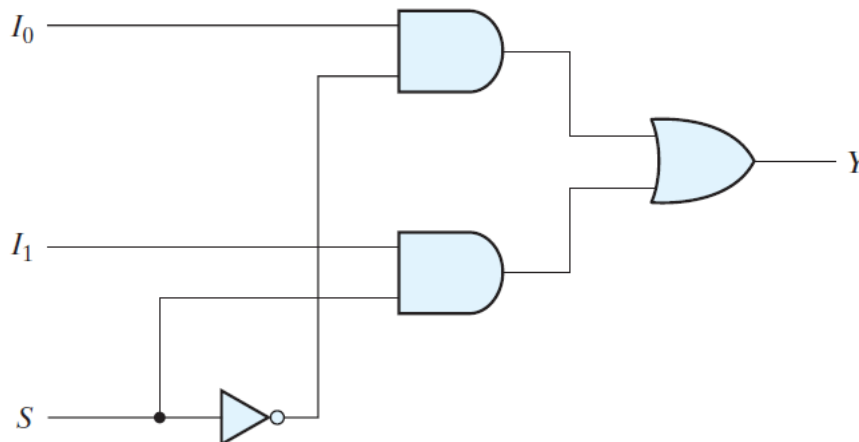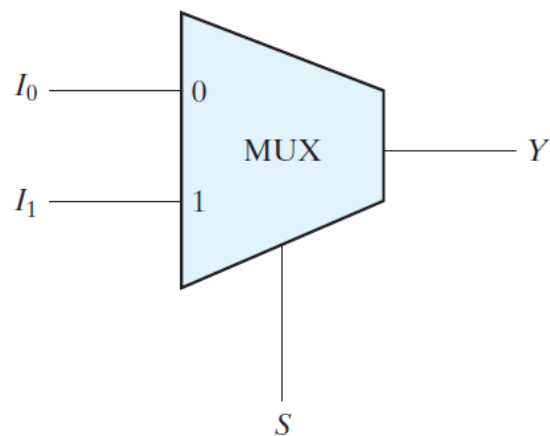

Function table


S	Y
0	I_0
1	I_1

Logic equation

$$Y = S'I_0 + SI_1$$


function table lists the input that is passed to the output for each combination of the binary selection values

4:1 MUX

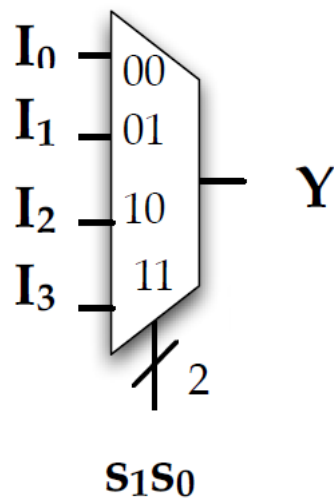

Function table

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

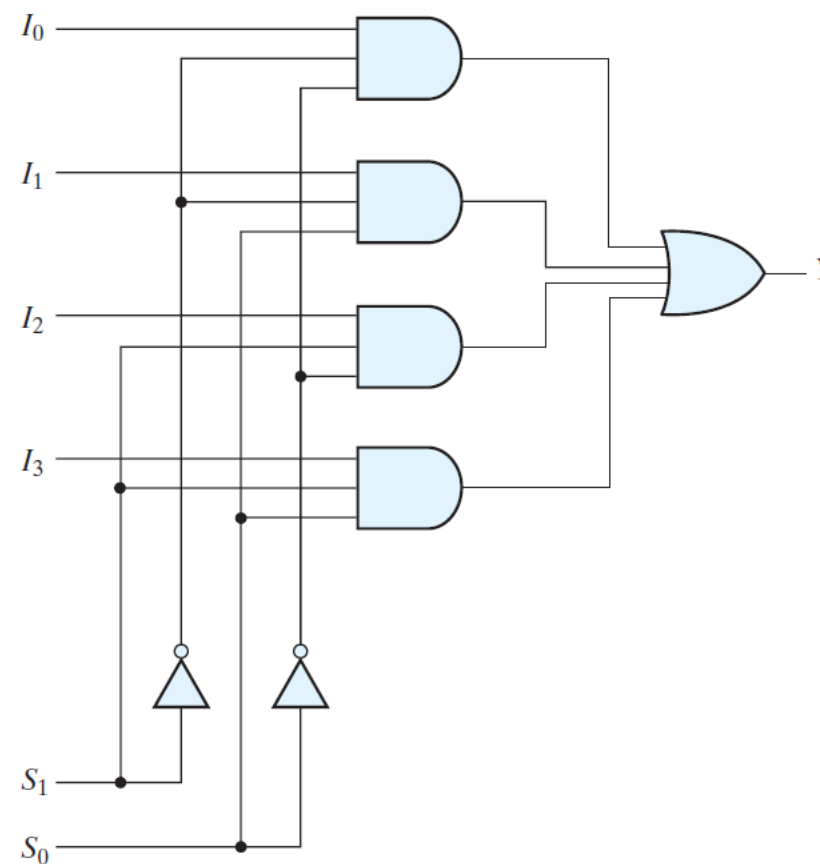


Logic equation

$$Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$$

For Internal Use Only!

MUX Composition

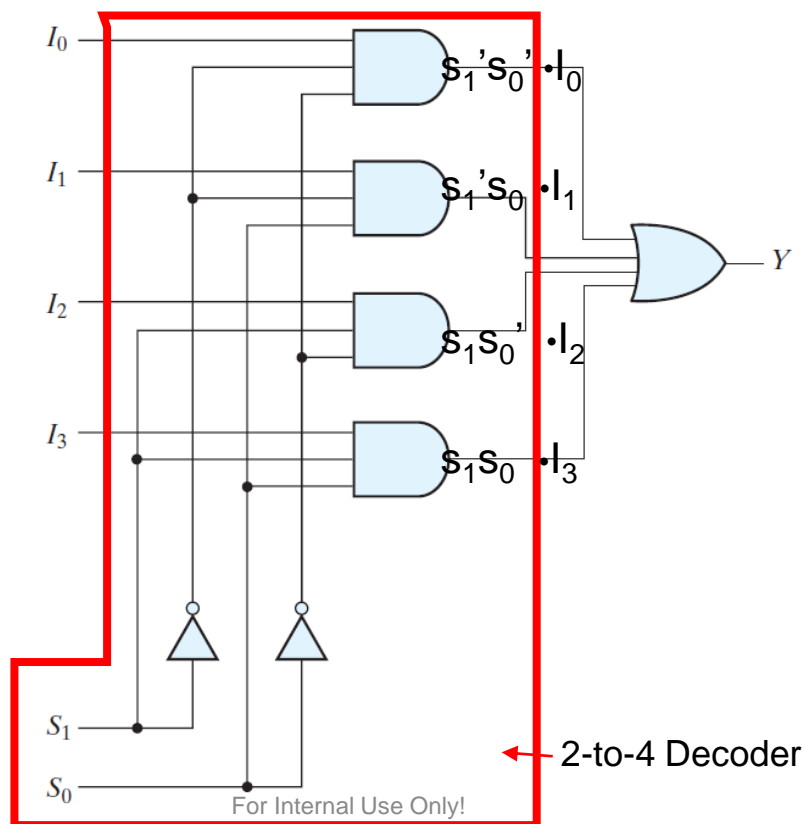- MUX = decoder + OR gate
 - The device has two control or selection lines S_1 and S_0 ,
 - Logic equation: $Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$




MUX for logic implementation Example1


- Implement AND function using MUX
 - can be used as a look-up table
 - 4:1 multiplexer can be used (truth table)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$Y = AB$

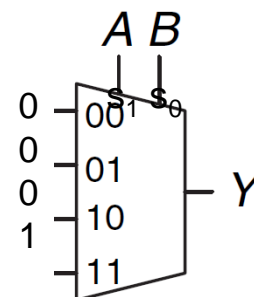

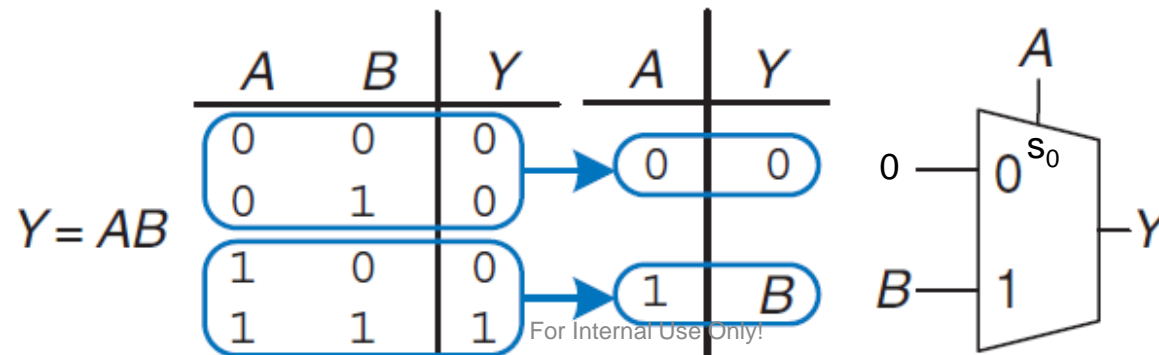- What if only 2:1 MUX is allowed to use?
 - By using variable as data inputs




MUX Exercise

- Exercise: Implement XNOR function using
 - 1) a 4:1 MUX
 - 2) a 2:1 MUX

MUX for logic implementation Example2



- Implement the function $Y(A,B,C) = \sum(0,3,4,5)$ with MUX

1. using 8:1 MUX

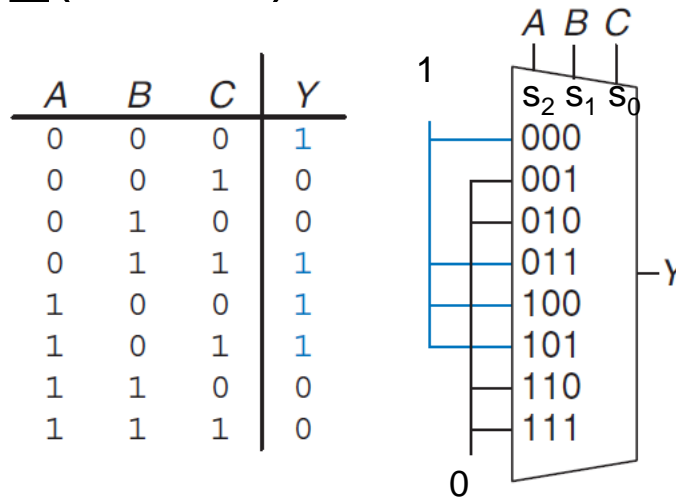

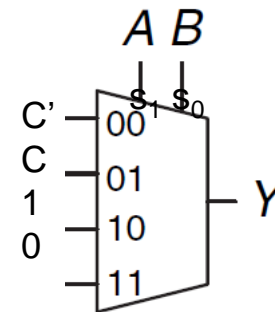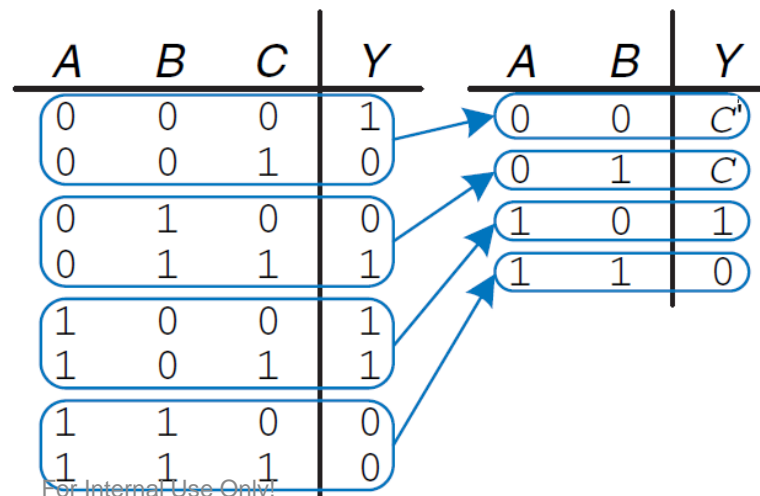2. using 4:1 MUX

- We can use 4:1 MUX by reducing the truth table to four rows by letting A,B as select bit s_1 and s_0




MUX for logic implementation Example2

- Implement the function $Y(A,B,C) = \sum(0,3,4,5)$ with MUX
- 3. Using 2:1 MUX?

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$Y = (B \oplus C)'$


$Y = B'$

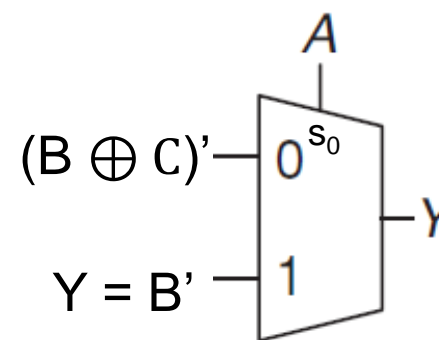

MUX for logic implementation Example3

- Implement $F(A, B, C, D) = (1, 3, 4, 11, 12, 13, 14, 15)$ with three selection inputs Multiplexer.
 - A must be connected to selection input S_2 so that A, B, and C correspond to selection inputs S_2, S_1 , and S_0 , respectively


A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

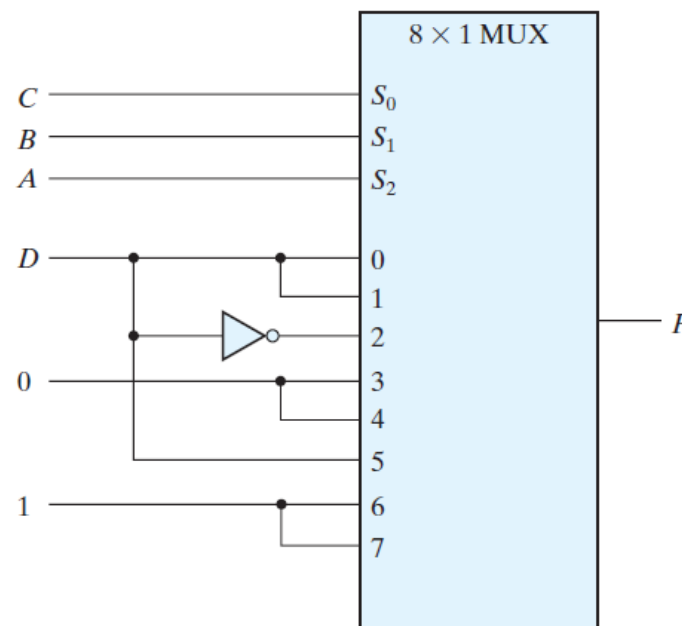


Quadruple 2:1 MUX (4-bit 2:1 MUX)

E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Function table

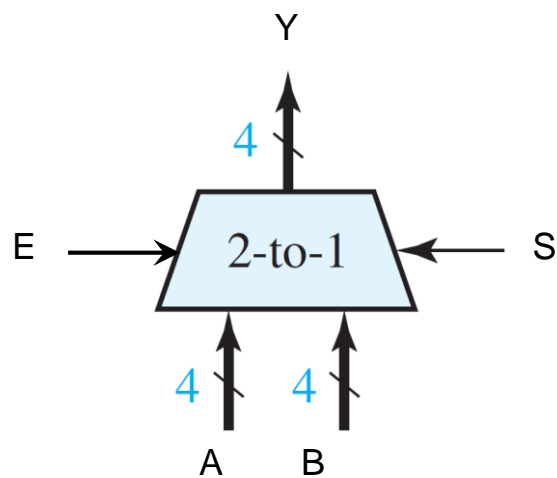

four 2:1 MUX with enable

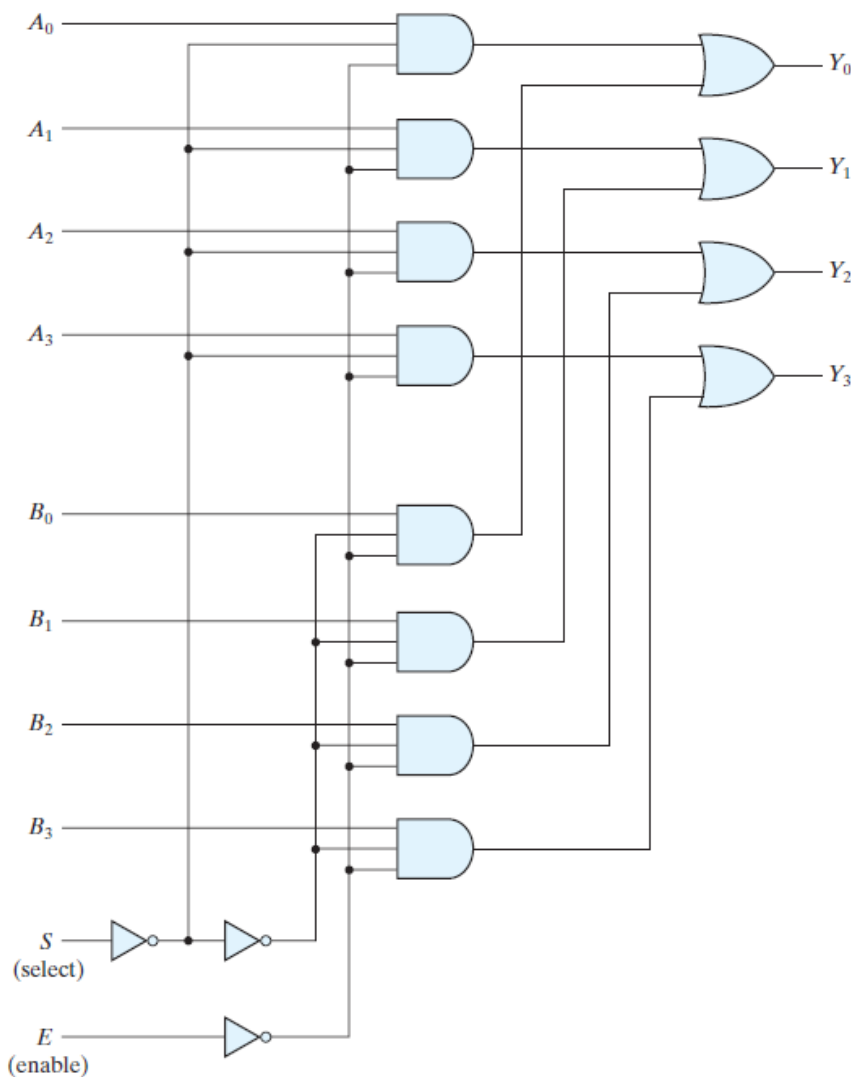

MUX Expansion

- Wider multiplexers, such as 8:1 and 16:1 multiplexers, can be built with smaller multiplexers

Function table


S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$f_1 = S_0'D_0 + S_0D_1$
 $f_2 = S_0'D_2 + S_0D_3$

Logic equation

$$\begin{aligned}
 Y &= s_1'f_1 + s_1f_2 \\
 &= s_1'(s_0'D_0 + s_0D_1) + s_1(s_0'D_2 + s_0D_3) \\
 &= s_1's_0'D_0 + s_1's_0D_1 + s_1s_0'D_2 + s_1s_0D_3
 \end{aligned}$$


4:1 MUX with three 2:1 MUX

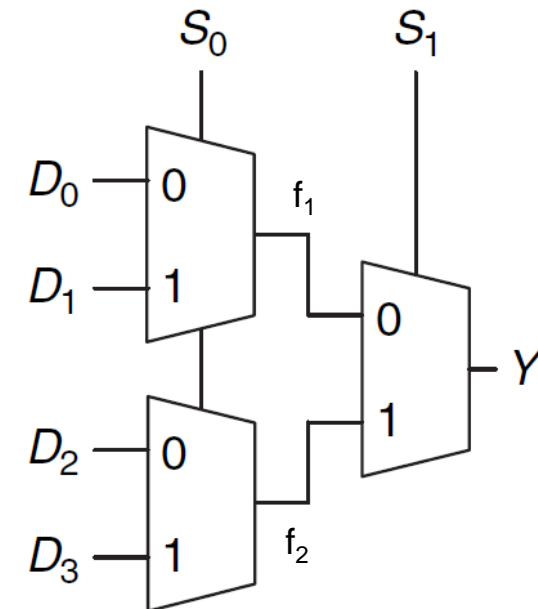

MUX Expansion



- How to build a 16-to-1 multiplexer using
 - $16 = 2^4$
 - 4 bits for selection

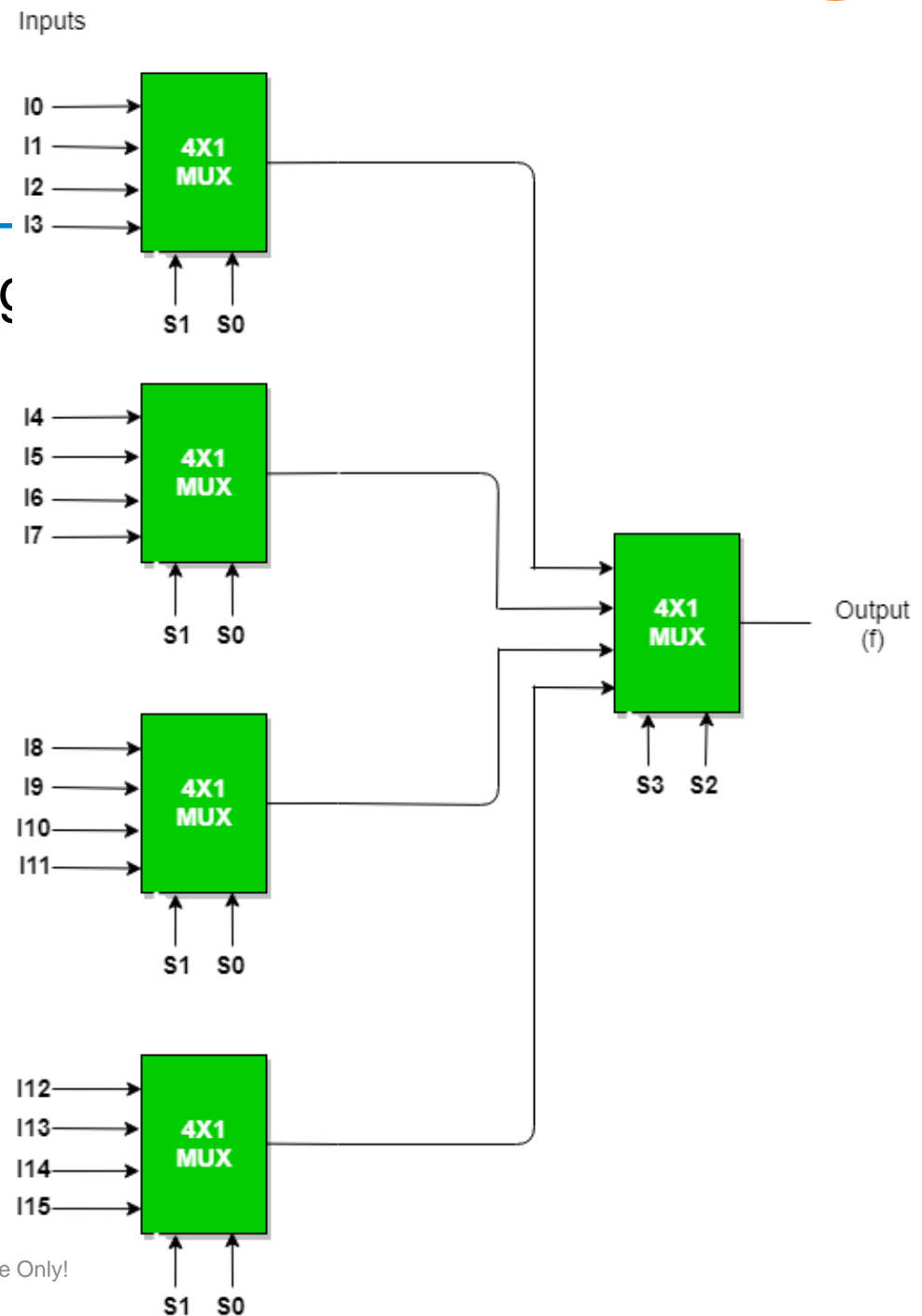Exercise: How to build a 8-to-1 multiplexer using two 4-to-1 MUX and a 2-to-1 MUX? You must carefully connect the selection and input pins



Demultiplexer

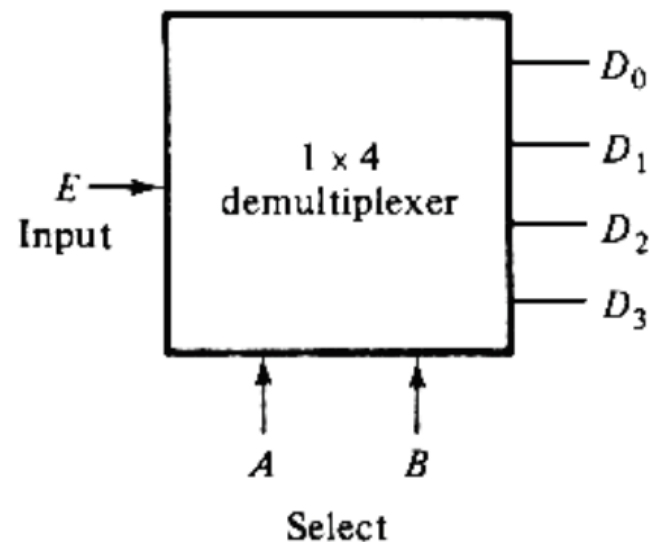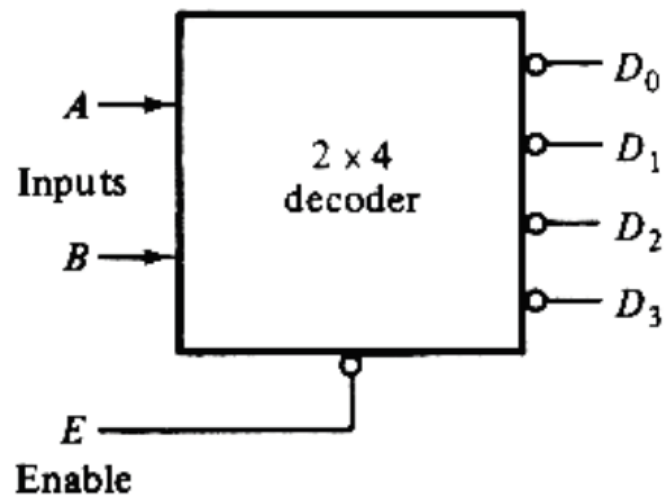- A decoder with enable input can function as demultiplexer
 - a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
 - Because decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a demultiplexer.




Outline

- Decoder
- Multiplexer
- **Encoder**

Encoder

- An encoder is an inverse of a decoder
- Encoder is a logic module that converts a **one-hot** input signal to a binary-encoded output signal
- Other input patterns are **forbidden** in the truth table
- Example: a 4- \rightarrow 2 encoder

a_3	a_2	a_1	a_0	b_1	b_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

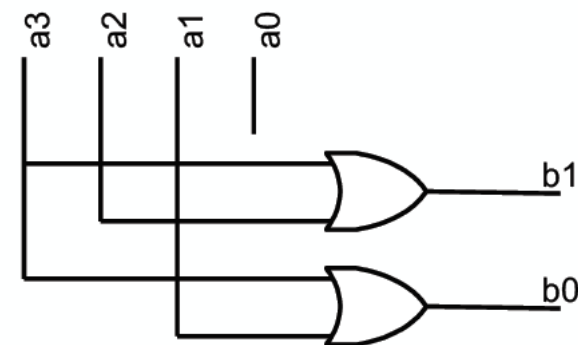

$$b_0 = a_3 + a_1$$

$$b_1 = a_3 + a_2$$

Encoder

- A combinational logic that performs the inverse operation of a decoder
 - Only one input has value 1 at any given time
 - Can be implemented with OR gates
- However, when both D3 and D6 goes 1, the output will be 111 (ambiguity)!

illegal inputs !Use priority encoder!

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$x = D_4 + D_5 + D_6 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$z = D_1 + D_3 + D_5 + D_7$$

Priority Encoder

- Ensure only one of the input is encoded
- Assuming D_3 has the highest priority, while D_0 has the lowest priority.
- X is the don't care conditions, V is the valid output indicator.

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

$$V = D_0 + D_1 + D_2 + D_3$$

Priority Encoder

D_0D_1		D_2D_3			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2 1
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8	m_9 1	m_{11} 1	m_{10} 1

$x = D_2 + D_3$


$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$


D_0D_1		D_2D_3			
		00	01	11	10
D_0	00	m_0 X	m_1 1	m_3 1	m_2
	01	m_4 1	m_5 1	m_7 1	m_6
	11	m_{12} 1	m_{13} 1	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11} 1	m_{10}

$y = D_3 + D_1 D_2'$


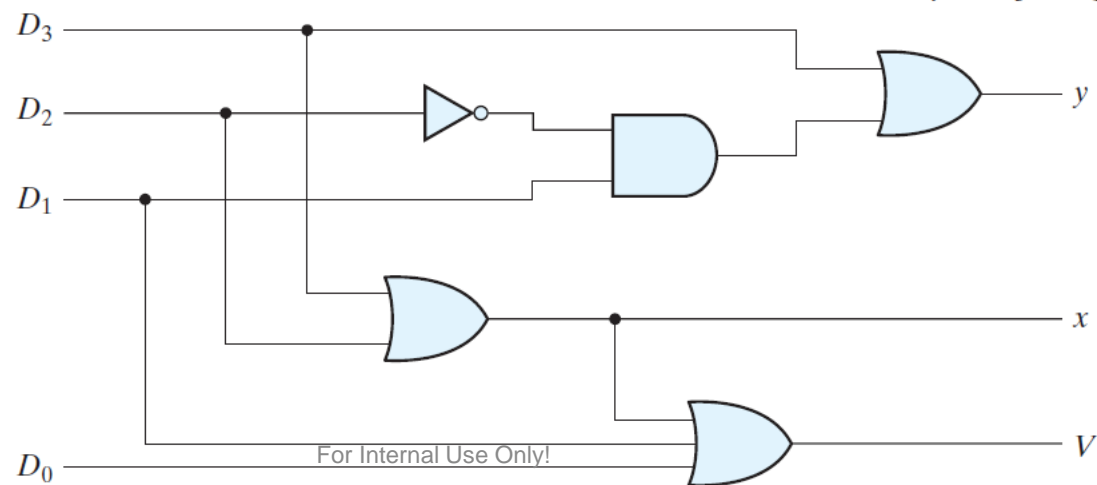


Tri-state

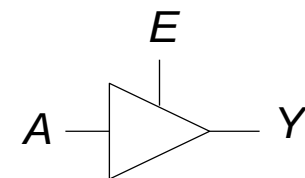- Tri-state driver (buffer) has three possible output states: 0, 1, Z (high impedance).



E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

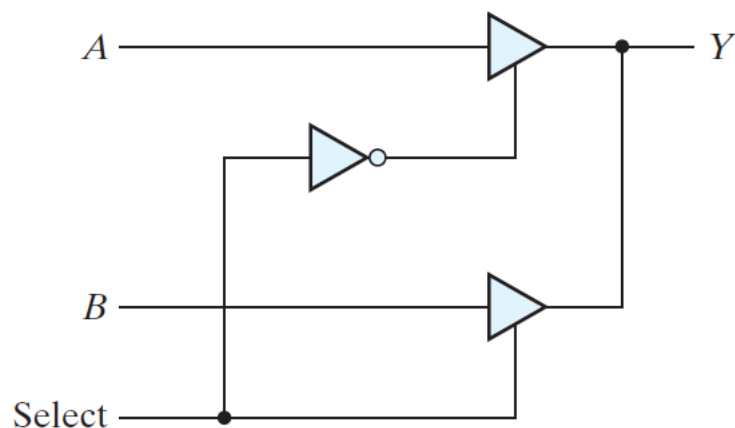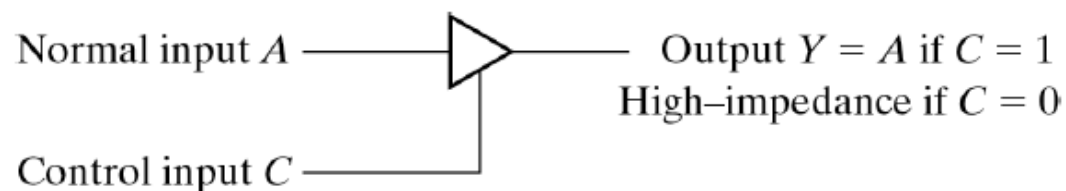


Sel	Y
0	A
1	B

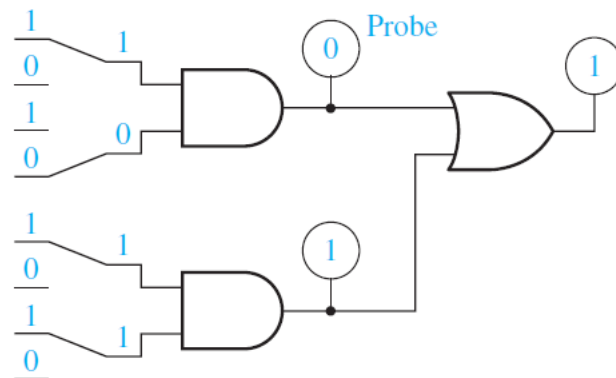
2:1 MUX using tri-state

Simulation and Testing of Logic Circuits

- For simulating logic circuits
 - Specify the circuit components and connections
 - Determine the circuit inputs
 - Observe the circuit outputs
- 4-valued logic simulator
 - 0 (low)、1 (high)、X (unknown)、Z (high impedance)



(a) Simulation screen showing switches

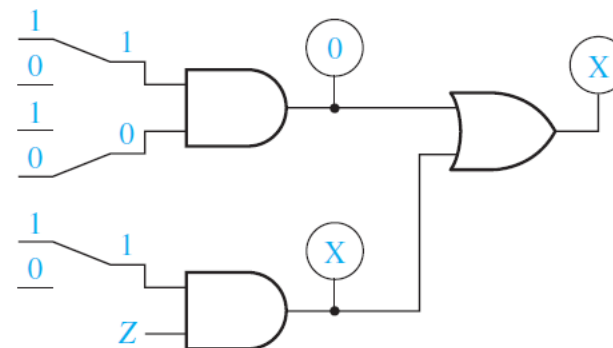

(b) Simulation screen with missing gate input

Simulation and Testing of Logic Circuits

- In the logic circuit, a wrong output may be due to
 - Verification
 - Incorrect design
 - Gates connected wrong
 - Wrong input signals to the circuit
 - Testing
 - Defective gates
 - Defective connecting wires

Simulation and Testing of Logic Circuits

- Logic circuit with incorrect output
 - $A = B = C = D = 1$, F should be 0 but an incorrect 1 is generated, what's wrong?

