

DIGITAL LOGIC(H)

Chapter 6 : Registers & Counters


2024 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.
Please do not repost it on other platforms without permission from the instructor.

Today's Agenda

- Recap
- Context
 - Registers
 - Design a sequence generator
 - Counters
 - Design a counter
- Reading: Textbook, Chapter 6.1-6.9

Recap

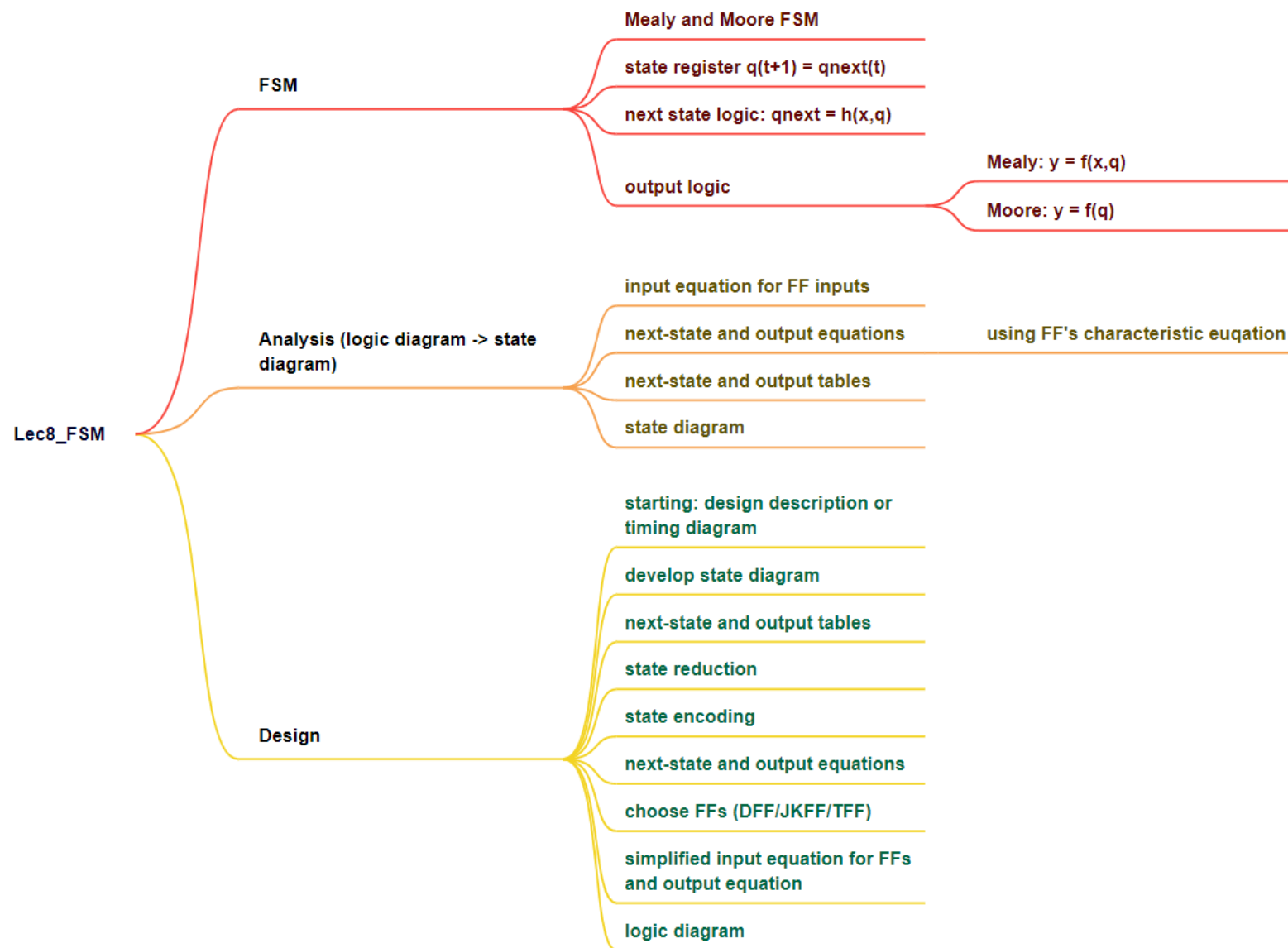


Outline

- **Various types of registers**
- Sequence generator with shift register
- Asynchronous counter
- Synchronous counter
- Design a synchronous counter

Clocked Sequential Circuits

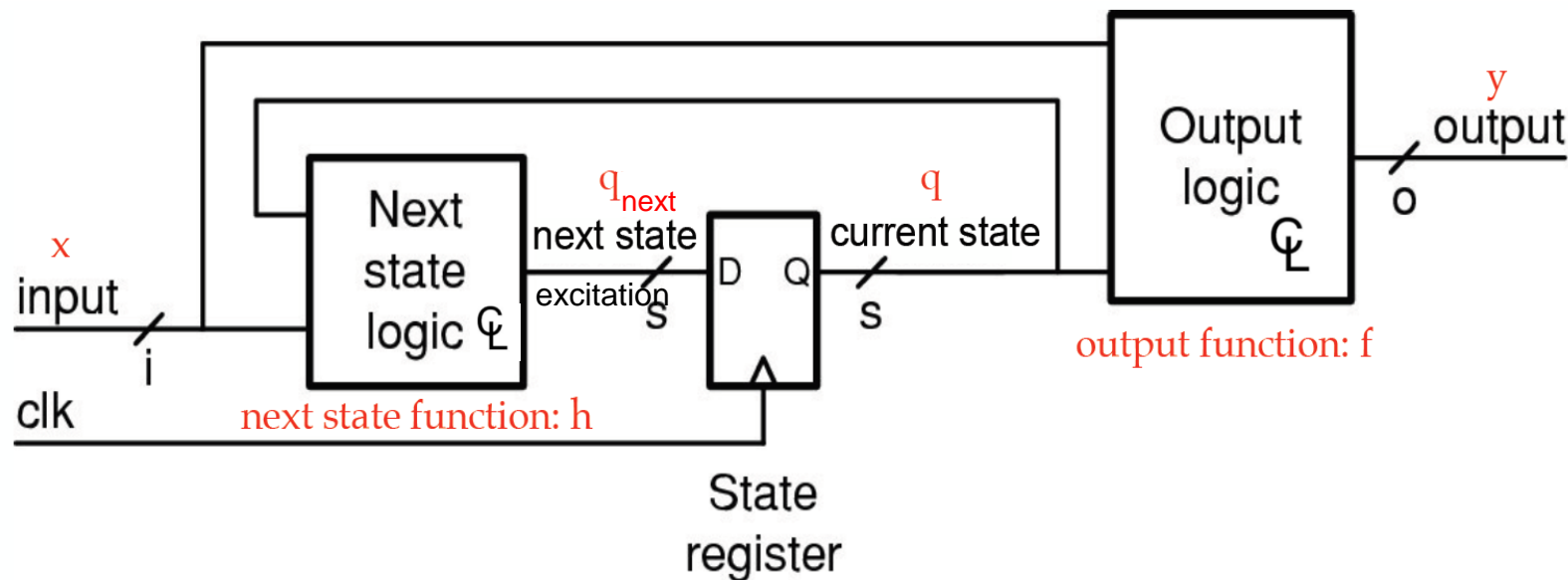- Clocked sequential circuits have flip-flops and combinational gates.
- FFs are essential, otherwise reduce to combinational.
- Circuits that include flip-flops are usually classified by the function they perform rather than by the name of the sequential circuit.
- Two such circuits are **registers** and **counters**.




Registers and Counters

- Register
 - A group of binary cells (FFs) suitable for holding binary data information
 - In addition to the FFs, a register may have combinational gates to control when and how the new information is transferred into the register (MUXes, ...)
- Counter
 - A register that goes through a predetermined sequence of states upon the application of input pulses
 - The gates in a counter are connected in such a way as to produce a pre-described sequence of binary states in the register (arithmetic circuits)

Shift Register


- Register: bitwise extension of a FF.
 - The shift register permits the stored data to move from a particular location to some other location within the register.
 - All the n FFs are driven by the common clock signal
 - sometimes with load control
- Type: Based on input & output
 - Serial-in to Serial-out (SISO)
 - Serial-in to Parallel-out (SIPO)
 - Parallel-in to Serial-out (PISO)
 - Parallel-in to Parallel-out (PIPO)
- Direction
 - Left shift
 - Right shift
 - Rotate (right or left)
 - Bidirectional
- Universal shift register

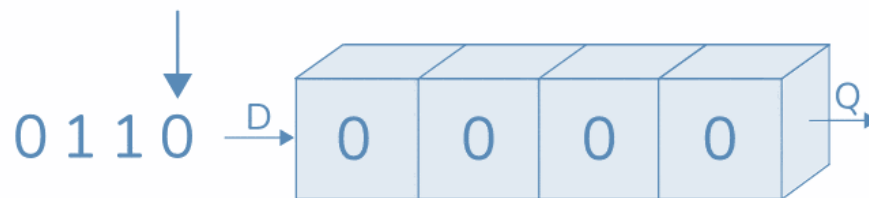

Bits moving through a SISO shift register

4-bit Serial-in to Serial-out

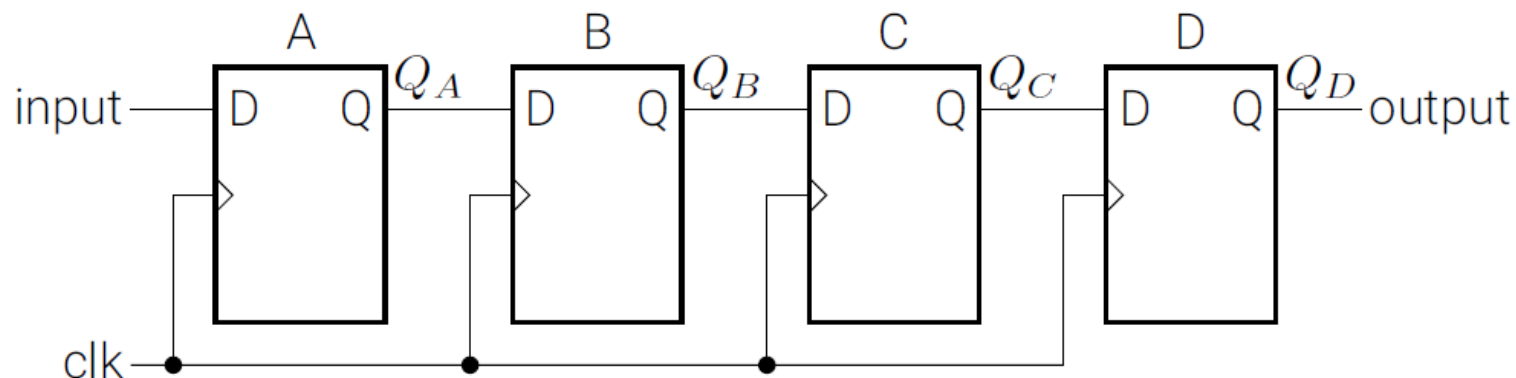- SISO: the data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control.




- An example of **1011** into the register. (Suppose bits are shifted in from LSB to MSB)

Starting from clock cycle 4, values could be read from Q_D one by one during each cycle

CLK	Q_A	Q_B	Q_C	Q_D output
initial	0	0	0	0
↑	1	0	0	0
↑	1	1	0	0
↑	0	1	1	0
↑	1	0	1	1

4-bit Serial-in to Parallel-out


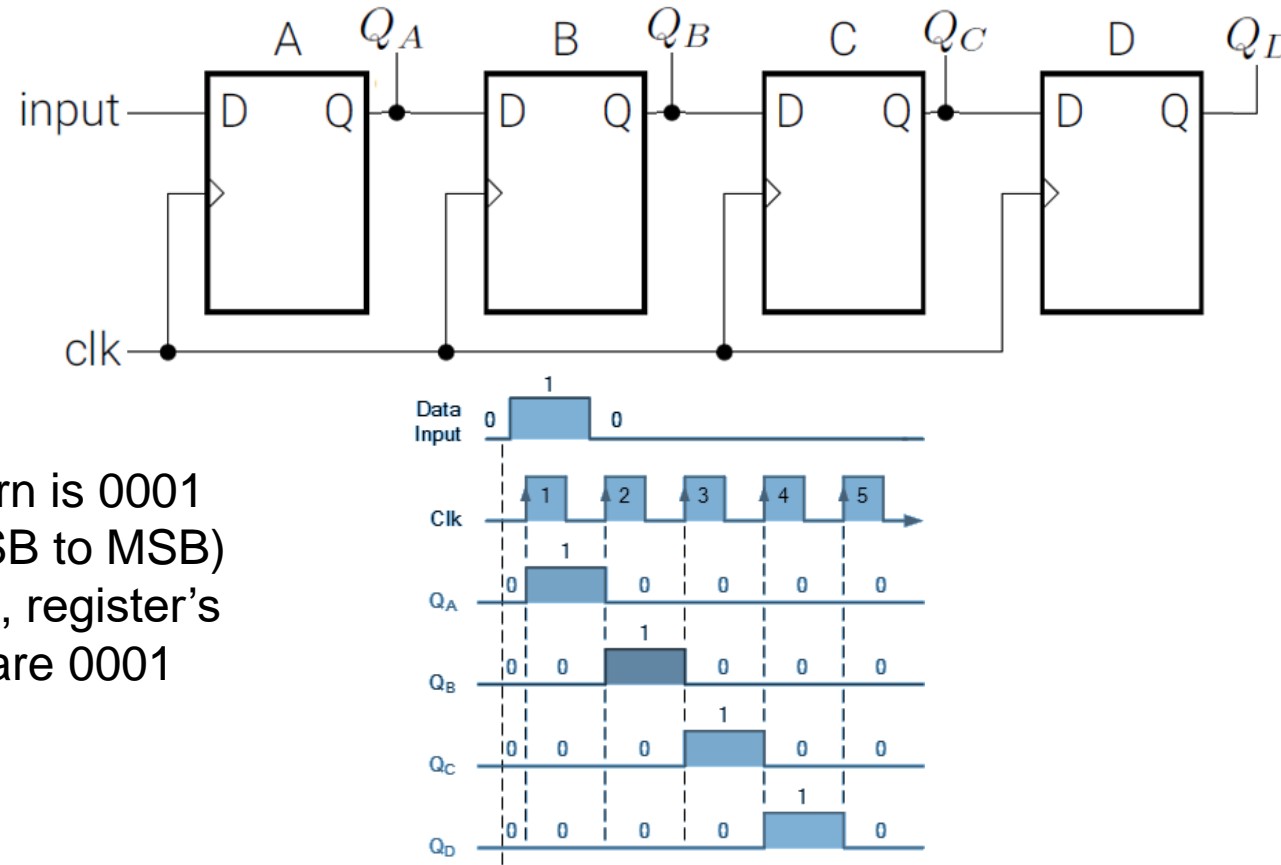
- SIPO: the register is loaded with serial data, one bit at a time, with the stored data being available at the output in parallel form.



Suppose input pattern is 0001
(values sent from LSB to MSB)
then at clock cycle 4, register's
outputs $Q_A Q_B Q_C Q_D$ are 0001


4-bit Parallel-in to Serial-out

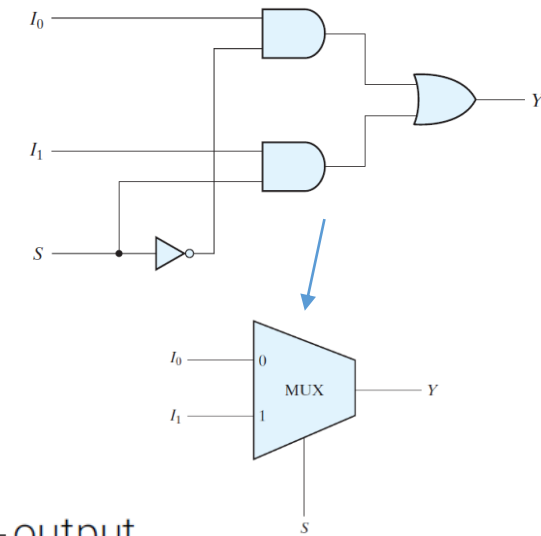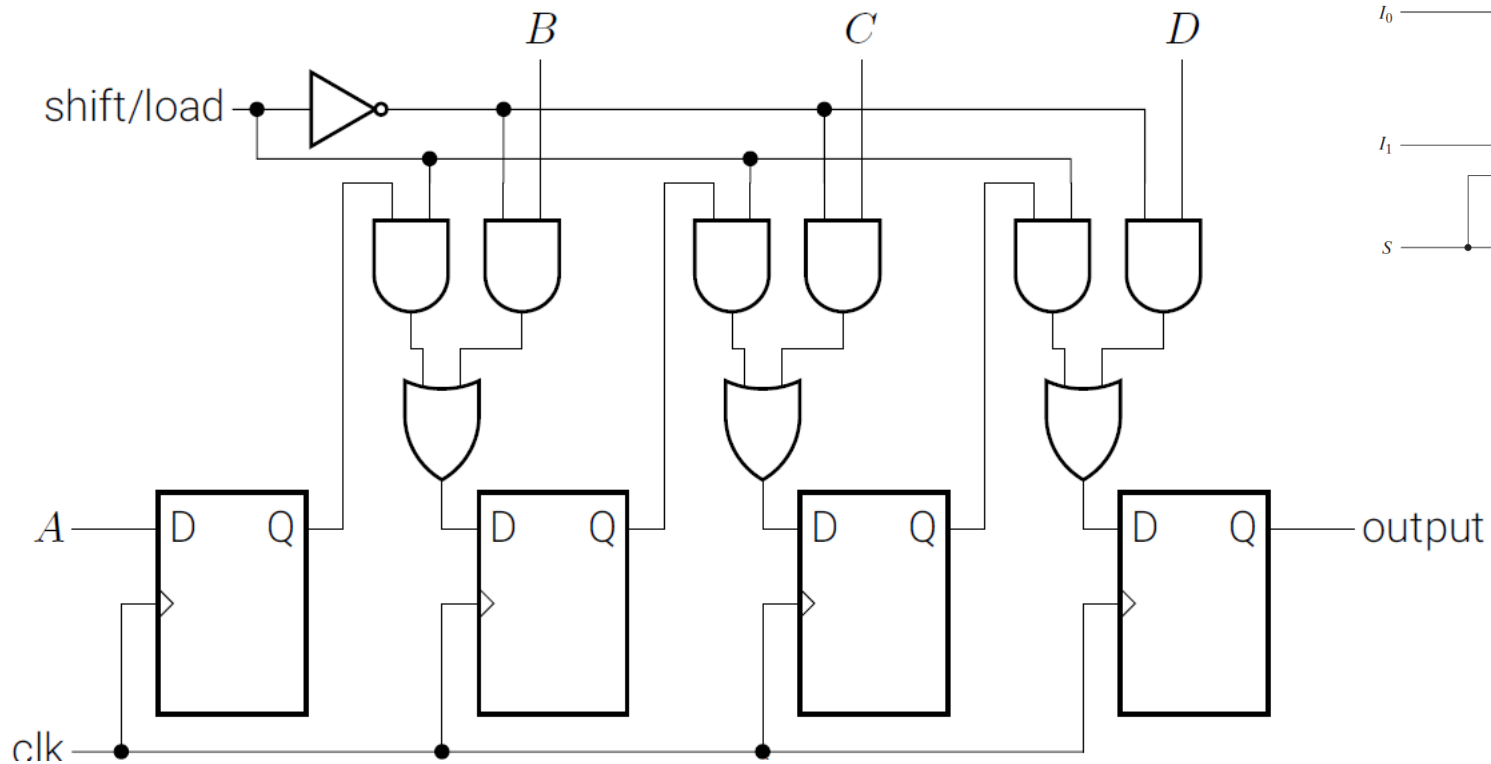- PISO: the parallel data is loaded into the register simultaneously and is shifted out of the register serially one bit at a time under clock control.



4-bit Parallel-in to Parallel-out

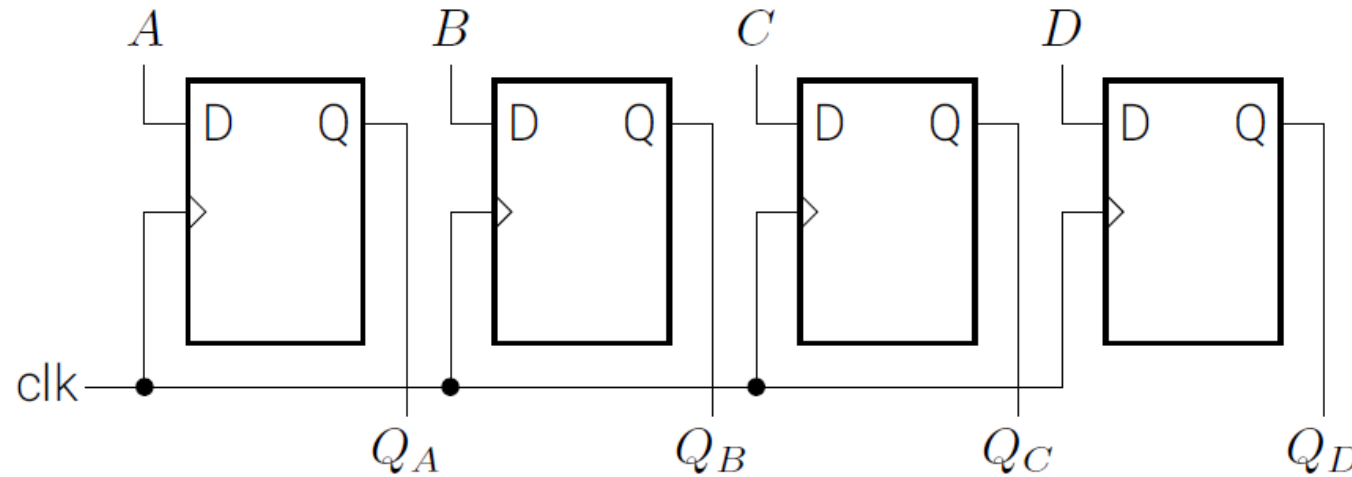- PIPO: the parallel data is loaded simultaneously into the register, and transferred together to their respective outputs by the same clock pulse.




PIPO with Parallel Load

- 4-bit Parallel-in to Parallel-out Register with Parallel Load Logic diagram

function table


Present state Load	Next state			
	Q_A	Q_B	Q_C	Q_D
0	No change			
1	A	B	C	D

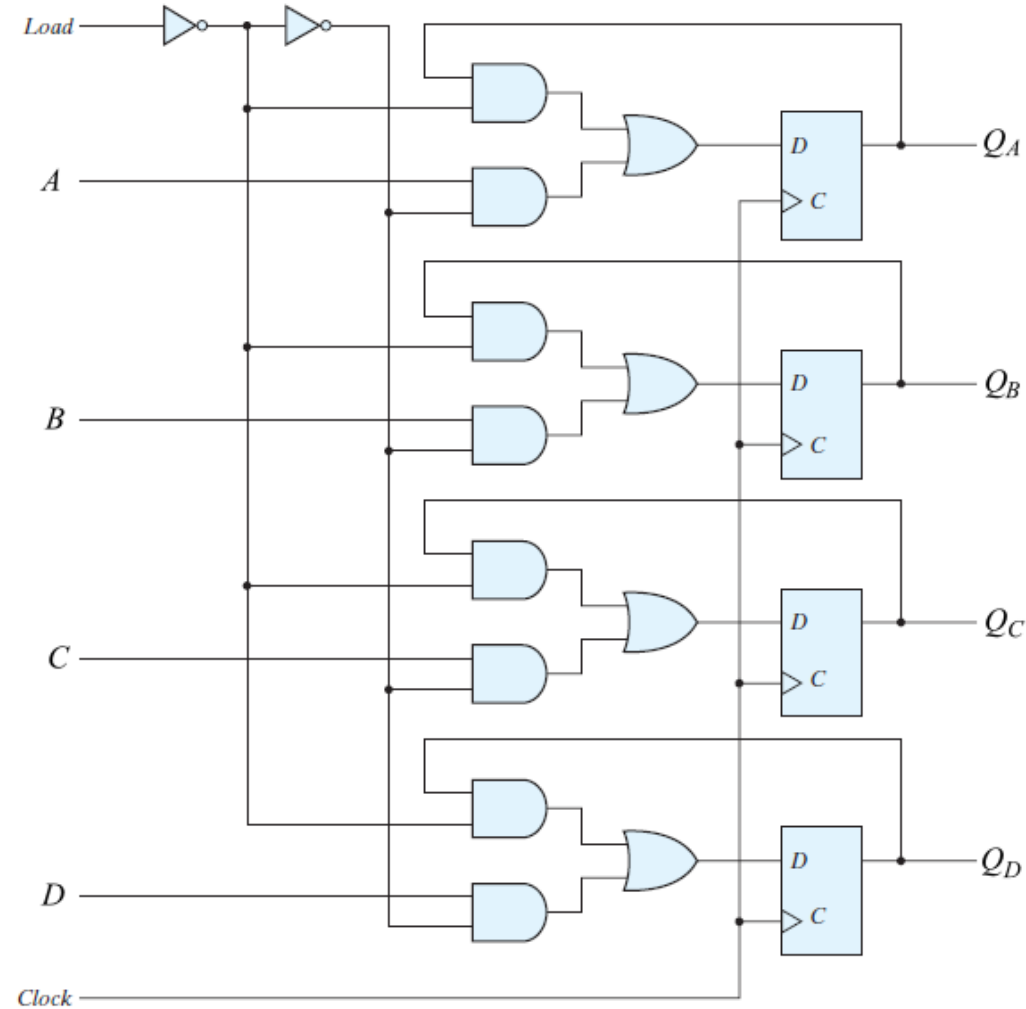

Universal Shift Register

- Universal shift register
 - Capable of both-direction shifting and parallel load/out


functional table

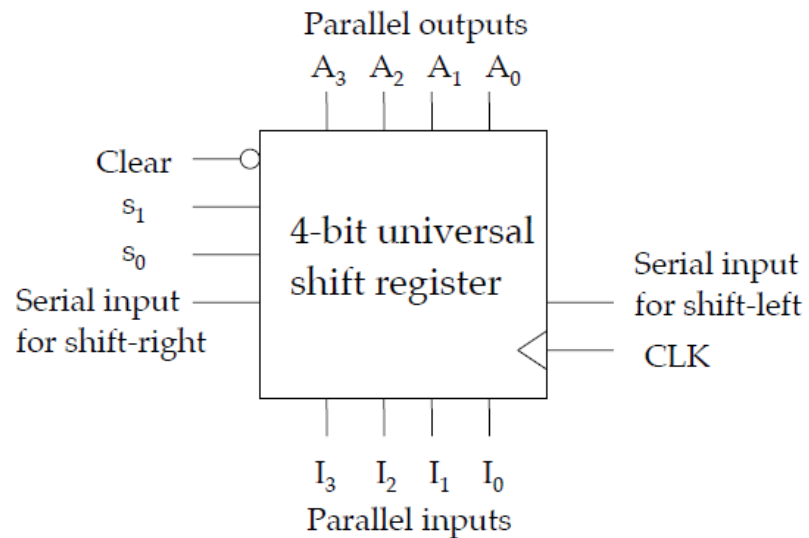

graphic symbol


Clear	S_1	S_0	A_3^+	A_2^+	A_1^+	A_0^+	Operation
0	x	x	0	0	0	0	Clear
1	0	0	A_3	A_2	A_1	A_0	No change
1	0	1	sri	A_3	A_2	A_1	Shift right
1	1	0	A_2	A_1	A_0	sli	Shift left
1	1	1	I_3	I_2	I_1	I_0	Parallel load

Universal Shift Register

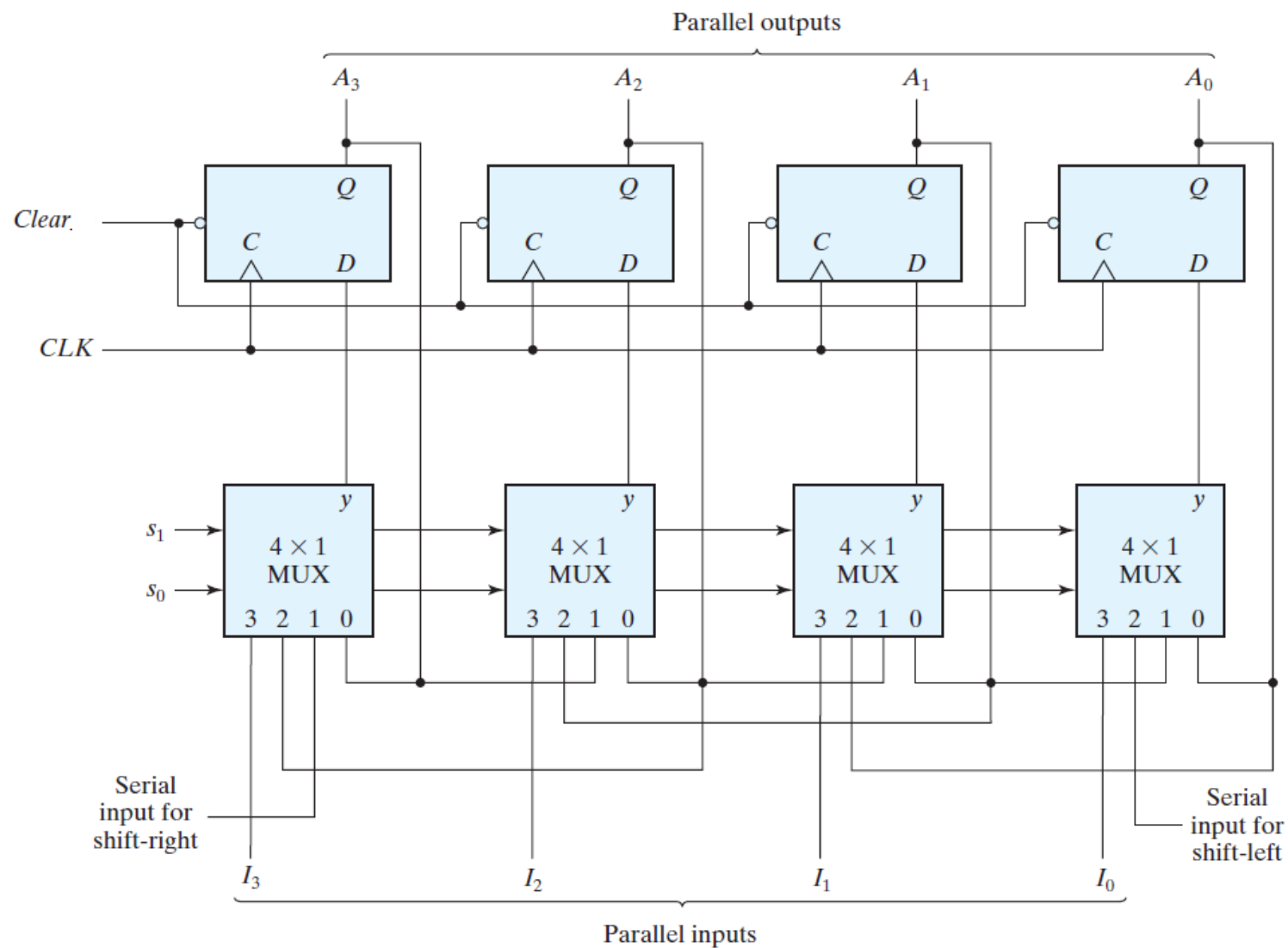


74 Series Shift Register

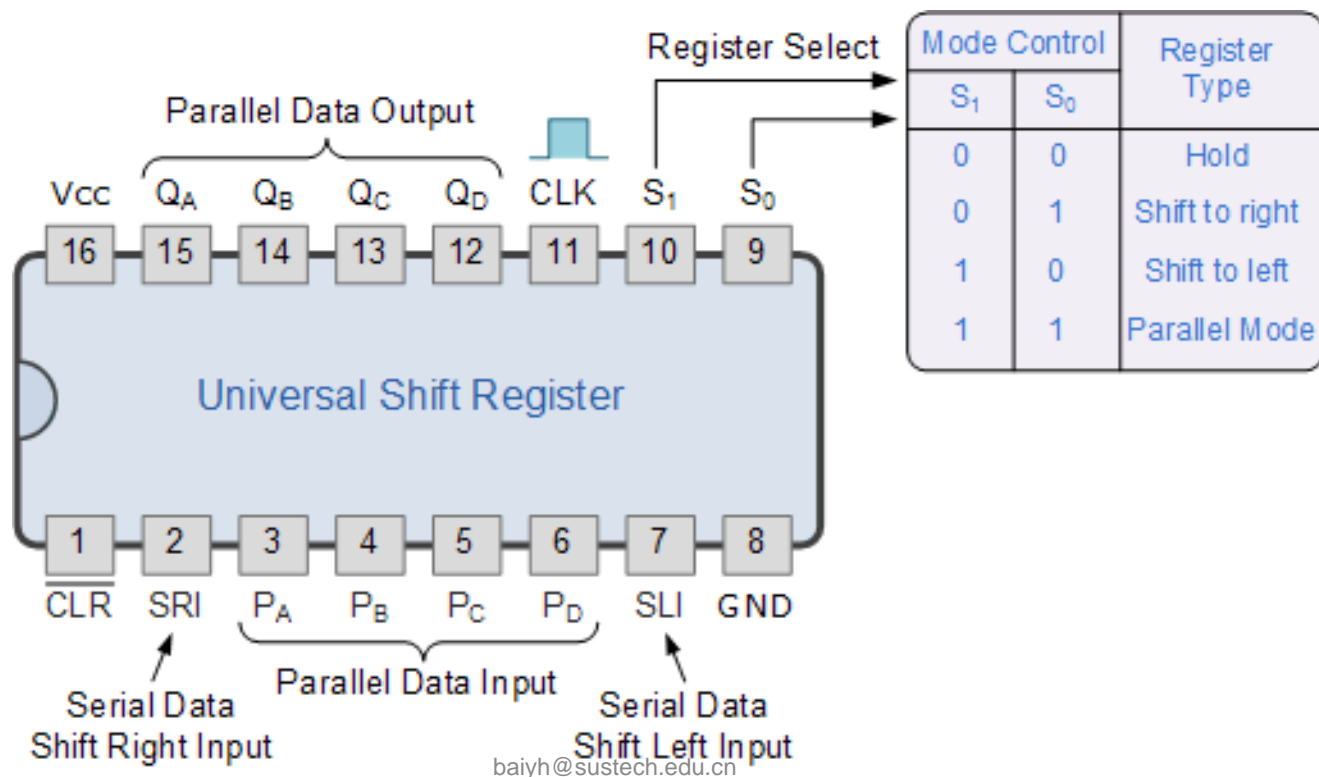- Some of the IC's available for shift registers
 - 74164 – 8-bit SIPO shift register
 - 74165 – 8-bit PISO shift register
 - 74194 – 4-bit PIPO shift register
 - 74195 – 4-bit Universal shift register (can be used for SISO, SIPO, and PIPO operations)




Serial/Parallel Transfer

 - Shifters are useful in serializers and deserialisers that convert data from parallel to serial form and back again





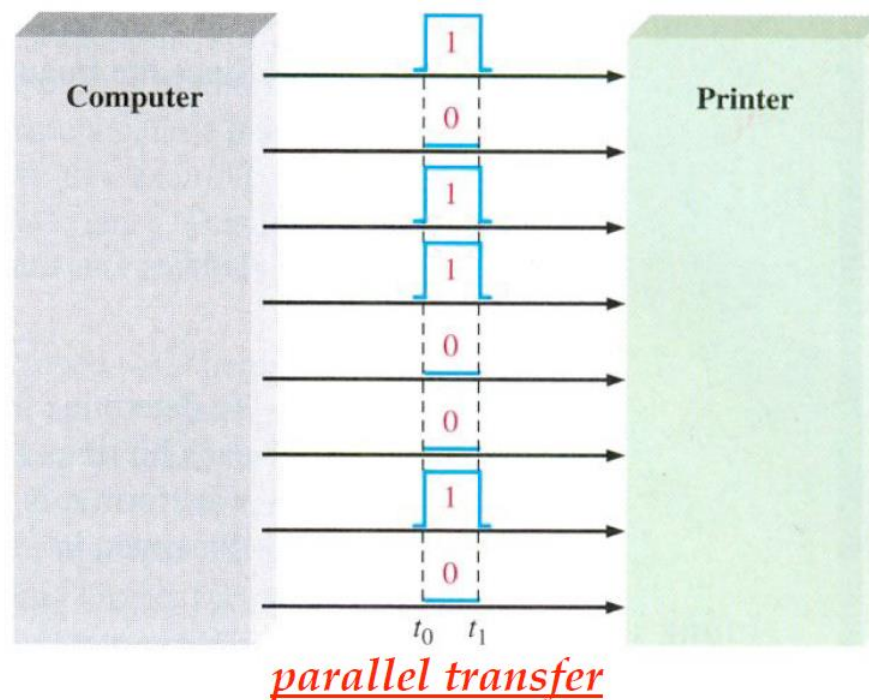- Serial
 - One bit a time
 - Need more time, low complexity
- Parallel
 - All bits at the same time
 - Transfer faster, higher complexity



Serial to Parallel Converter

- clk for SIPO is faster

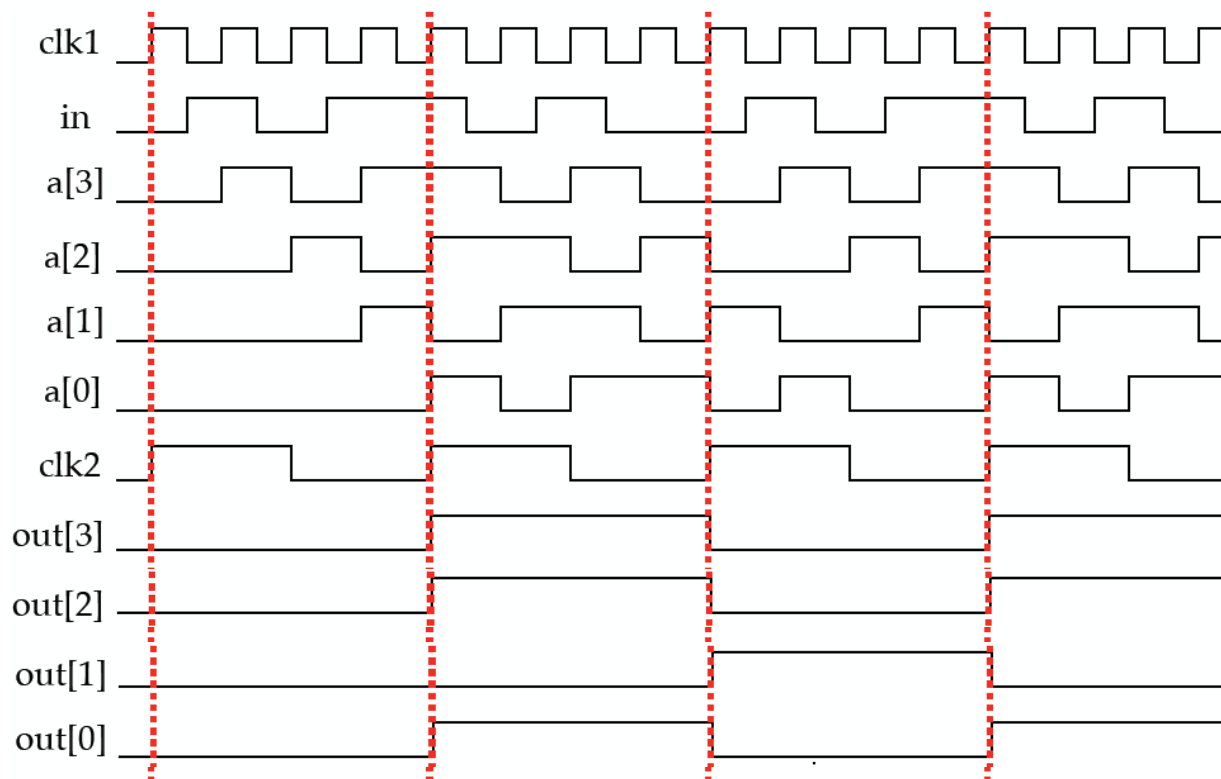 


Outline

- Various types of registers
- **Sequence generator with shift register**
- Asynchronous counter
- Synchronous counter
- Design a synchronous counter



Sequence Generator

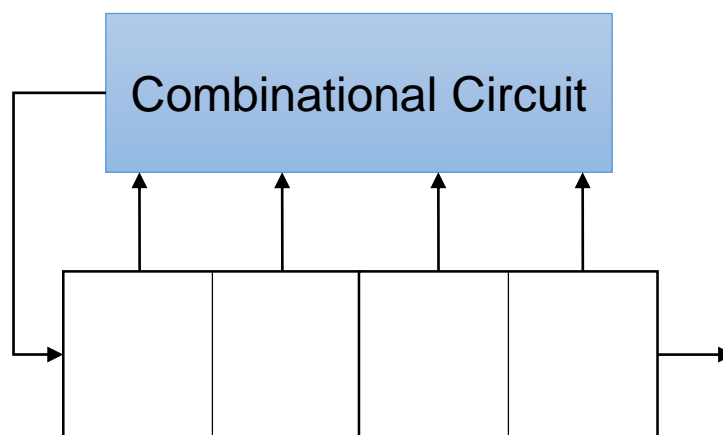- A sequence generator is a circuit that generates a desired sequence of bits in synchronization with a clock.
- Can be used as a random bit generator, code generator, and prescribed period generator.
- The output of the combinational circuit is a function of the shift register state and is connected to the serial input of the shift register





Sequence Generator

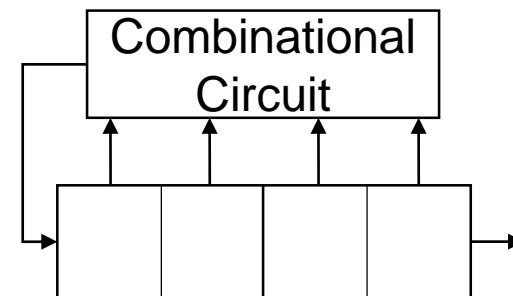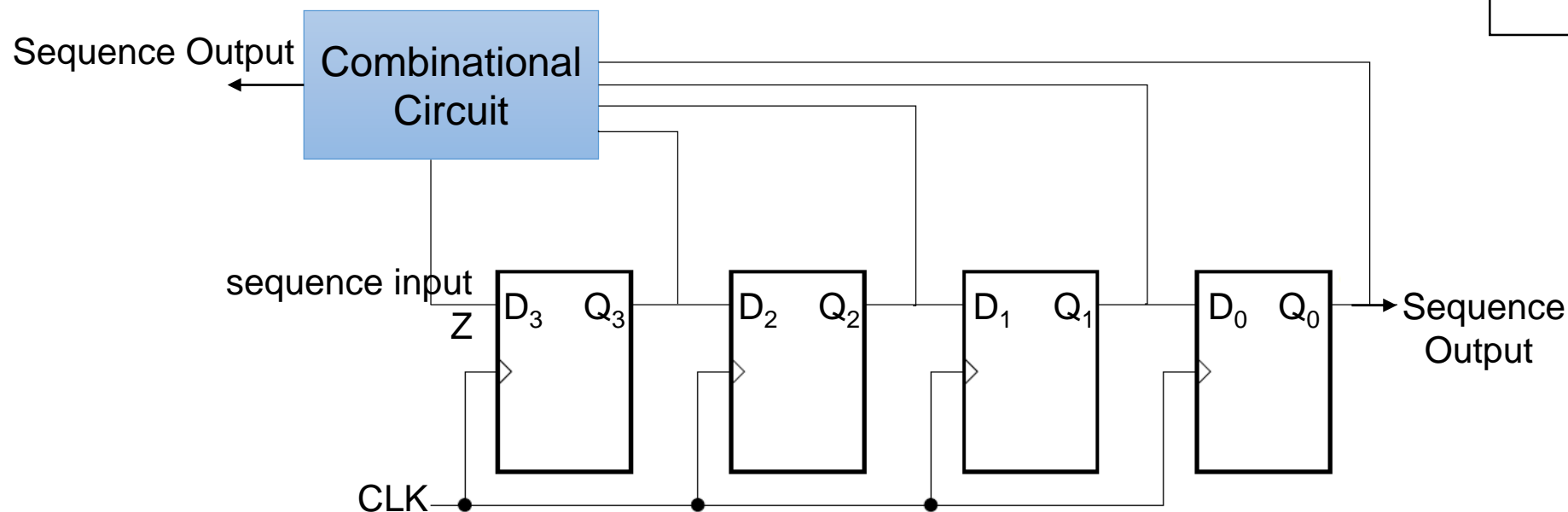- n FFs can generate a sequence with the length of $N \leq 2^n - 1$
- The required sequence can be obtained from the output of any FF, or the output of the combinational circuit



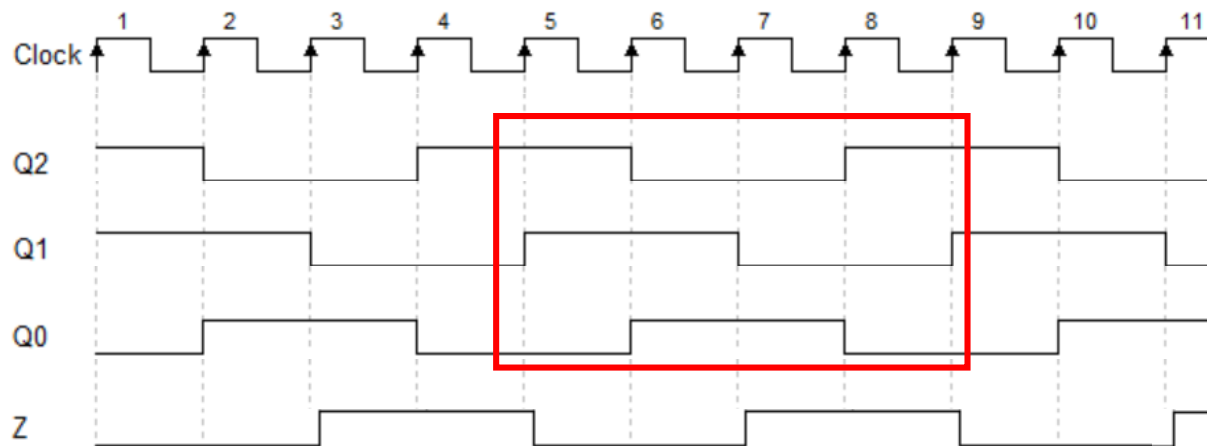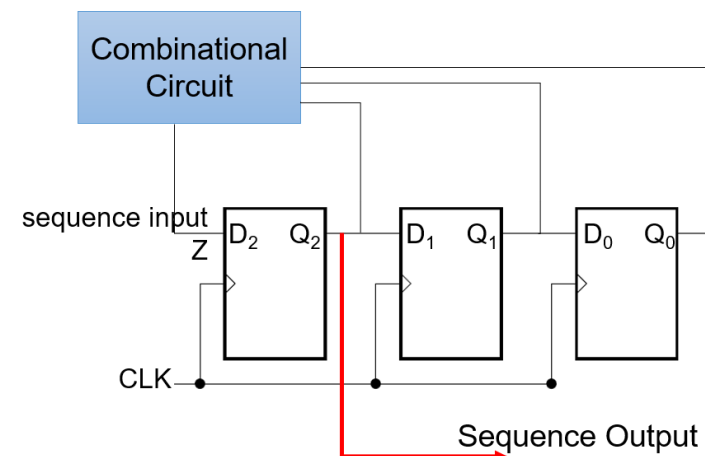Example: Design a 4-bit Sequence Generator

- Design of a sequence generator to generate a sequence of **1001**. (MSB is first generated)
 - The minimum number of flip-flops required to generate a sequence of length N is given by $N \leq 2^n - 1 \rightarrow n = 3$ (3 FFs)
 - Noted all zero's state is excluded to avoid that circuit being stuck in this state.



	FF's outputs			Serial Input
Clk	Q ₂	Q ₁	Q ₀	Z
↑	1	1	0	
↑	0	1	1	
↑	0	0	1	
↑	1	0	0	

Example: Design a 4-bit Sequence Generator


- Design of a sequence generator to generate a sequence of **1001**. (MSB is first generated)
 - The minimum number of flip-flops required to generate a sequence of length N is given by $N \leq 2^n - 1 \rightarrow n = 3$ (3 FFs)

CLK	Z	Q_2	Q_1	Q_0
↑	0	1	1	0
↑	0	0	1	1
↑	1	0	0	1
↑	1	1	0	0

CLK	Q_2	Q_1	Q_0	Z
↑	1	1	0	0
↑	0	1	1	0
↑	0	0	1	1
↑	1	0	0	1

Q_1Q_0		00	01	11	10
Q_2	0	X	1	0	X
	1	1	X	X	0


$$Z = Q_1'$$

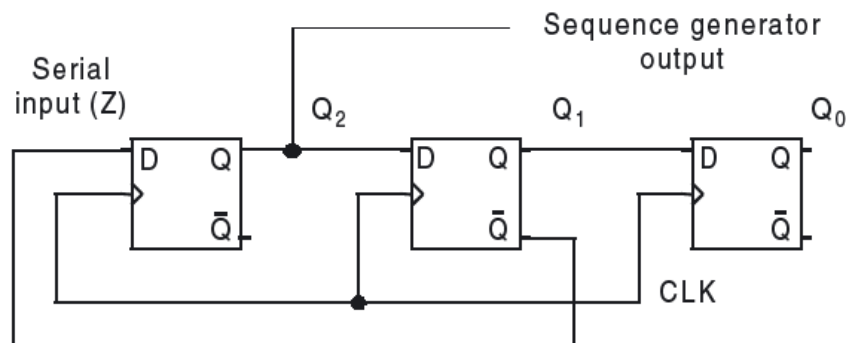


Example: Design a 5-bit Sequence Generator

- Design of a sequence generator to generate a sequence of **10011**. (MSB is first generated)
 - The minimum number of flip-flops required to generate a sequence of length N is given by $N \leq 2^n - 1 \rightarrow n = 3$ (3 FFs)

	FF's outputs			Serial Input
CLK	Q_2	Q_1	Q_0	Z
↑	1	1	1	0
↑	0	1	1	0
↑	0	0	1	1
↑	1	0	0	1
↑	1	1	0	1

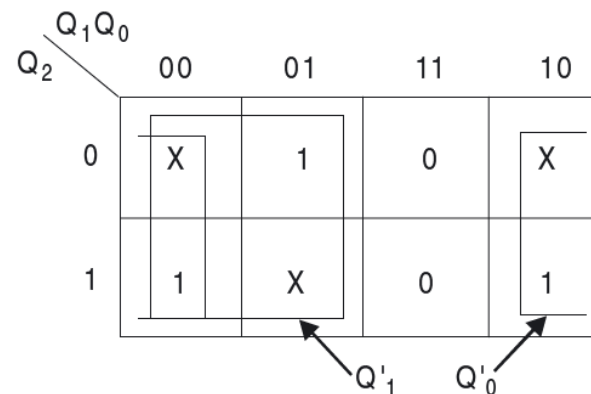

$$Z = Q_1' + Q_0'$$

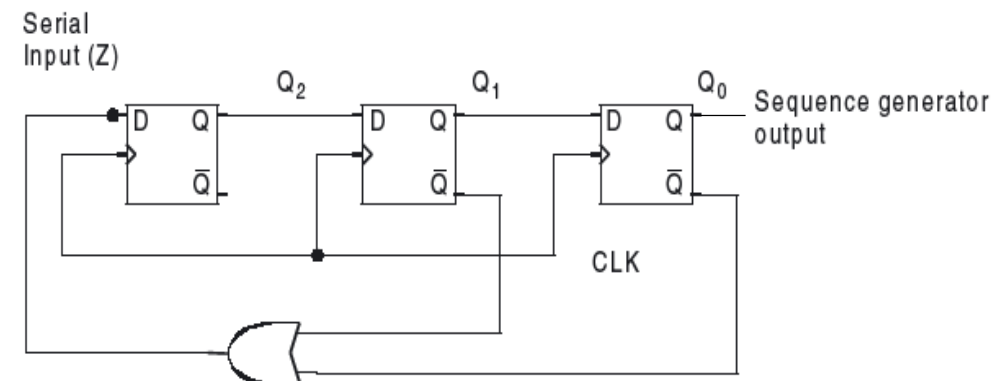

Example: Design a 6-bit Sequence Generator

- Design of a sequence generator to generate a sequence of **110101**(MSB is first generated)
 - The minimum number of flip-flops required to generate a sequence of length N is given by $N \leq 2^n - 1$
 - The minimum value of n to satisfy the above condition is 3.

CLK	Q_2	Q_1	Q_0	Z
↑	1	1	0	
↑	1	1	1	
↑	0	1	1	
↑	1	0	1	
↑	0	1	0	
↑	1	0	1	

State 101 occurs twice!

3 flip-flops are not sufficient to generate the given sequence.


Example: Design a 6-bit Sequence Generator

- Needs 4 FFs to generate 110101

clk	Q_3	Q_2	Q_1	Q_0	Z
↑	1	1	0	1	1
↑	1	1	1	0	0
↑	0	1	1	1	1
↑	1	0	1	1	0
↑	0	1	0	1	1
↑	1	0	1	0	1

		$Q_1 Q_0$		Q_1	
		00	01	11	10
$Q_3 Q_2$	00	X	X	X	X
	01	X	1	1	X
	11	X	1	X	0
	10	X	X	0	1
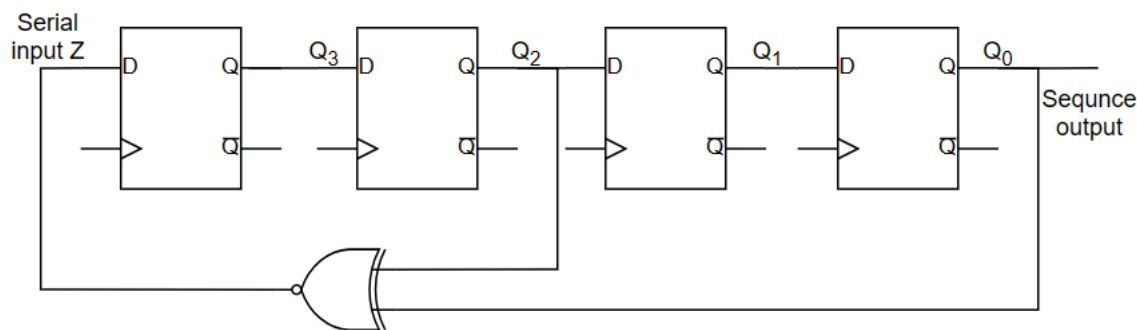
$$Z = Q_2 Q_0 + Q_2' Q_0' = (Q_2 \oplus Q_0)'$$



Outline

- Various types of registers
- Sequence generator with shift register
- **Asynchronous counter**
- Synchronous counter
- Design a synchronous counter

Counters

- A counter is a special type of register that counts upward, downward, or in any pre-specified sequence
 - Ripple counters (asynchronous counter)
 - The output transition of flip-flop serves as a source for triggering other flip-flops
 - Synchronous counters
 - The clock inputs of all flip-flops receive a common clock

Asynchronous Counters

- aka. Serial or ripple counters
- All the flip-flops are not driven by the same clock pulse.
 - The successive flip-flop is triggered by the output of the previous flip-flop.
 - Hence the counter has cumulative settling time, which limits its speed of operation




4-bit Binary Ripple Counter


- Binary Up count sequence

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

- Timing diagram


 


baiyh@sustech.edu.cn

 


4-bit Binary Ripple Counter

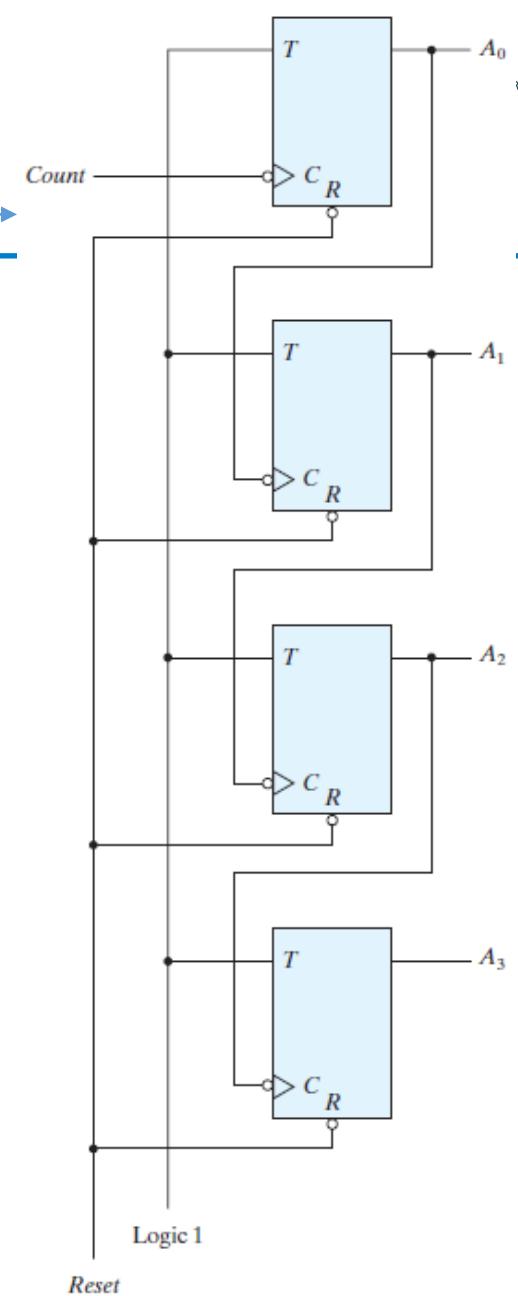 
- Binary Up counter using TFF
- What if design a down counter?
 - just replace negative-edge triggered clock with positive-edge triggered clock



BCD Ripple Counter

 


Present State				Next State			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

 

Three-decade BCD Ripple Counter

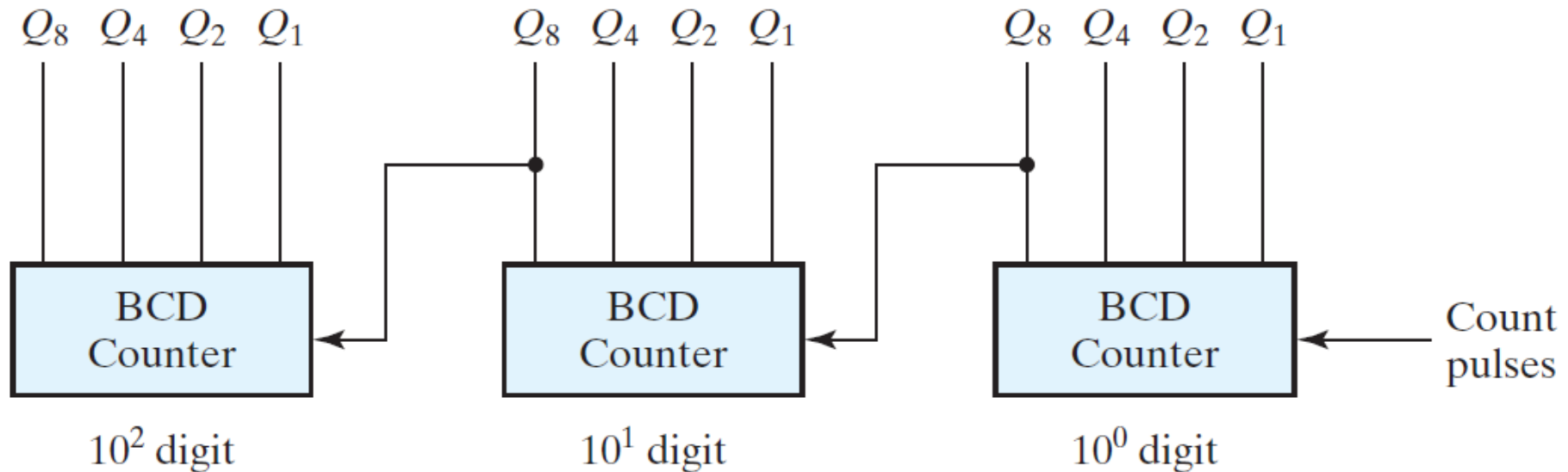- When Q_8 in one decade goes from 1 to 0, it triggers the count for the next higher decade while it's own decade goes from 9 to 0.



Outline

- Various types of registers
- Sequence generator with shift register
- Asynchronous counter
- **Synchronous counter**
- Design a synchronous counter


Synchronous counters

- The ripple or asynchronous counter is the simplest to build, but its highest operating frequency is limited because of ripple action.
 - delay time
 - glitches
- Both of these problems can be overcome, if all the flip-flops are clocked synchronously.
- The resulting circuit is known as a synchronous counter.

4-bit Synchronous Binary Counters


- Count up
 - As the number of stages increases, the number of AND gates also increases, along with the number of inputs for each of those AND gates.

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

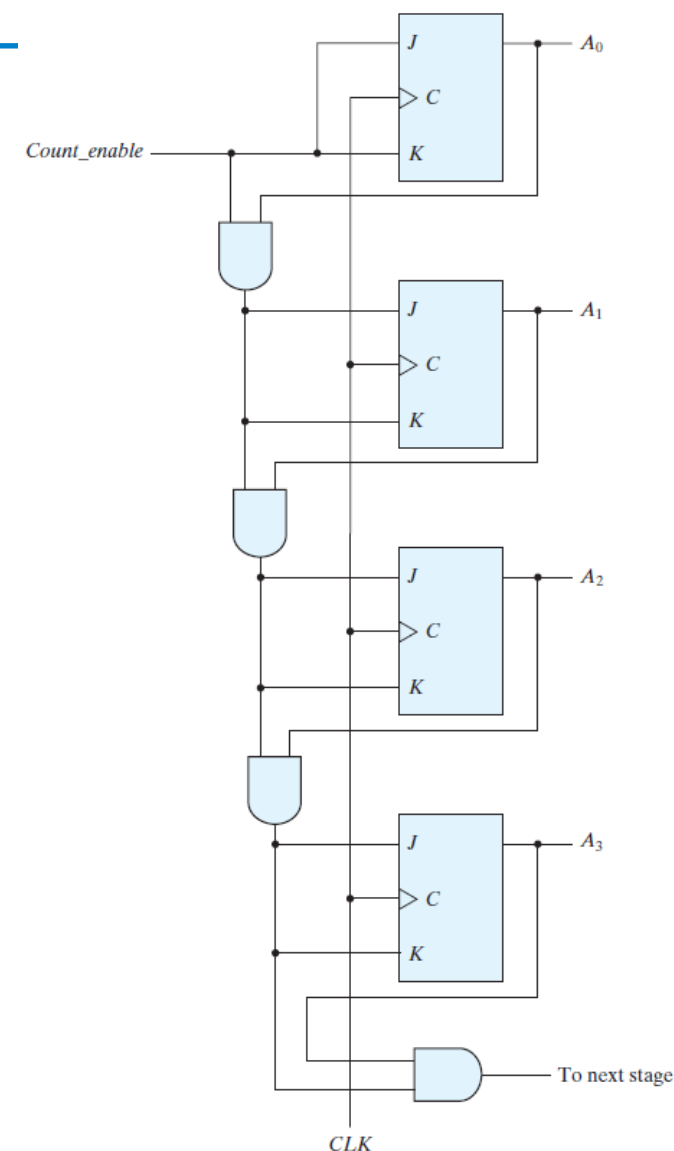

4-bit Up/Down Binary Counter

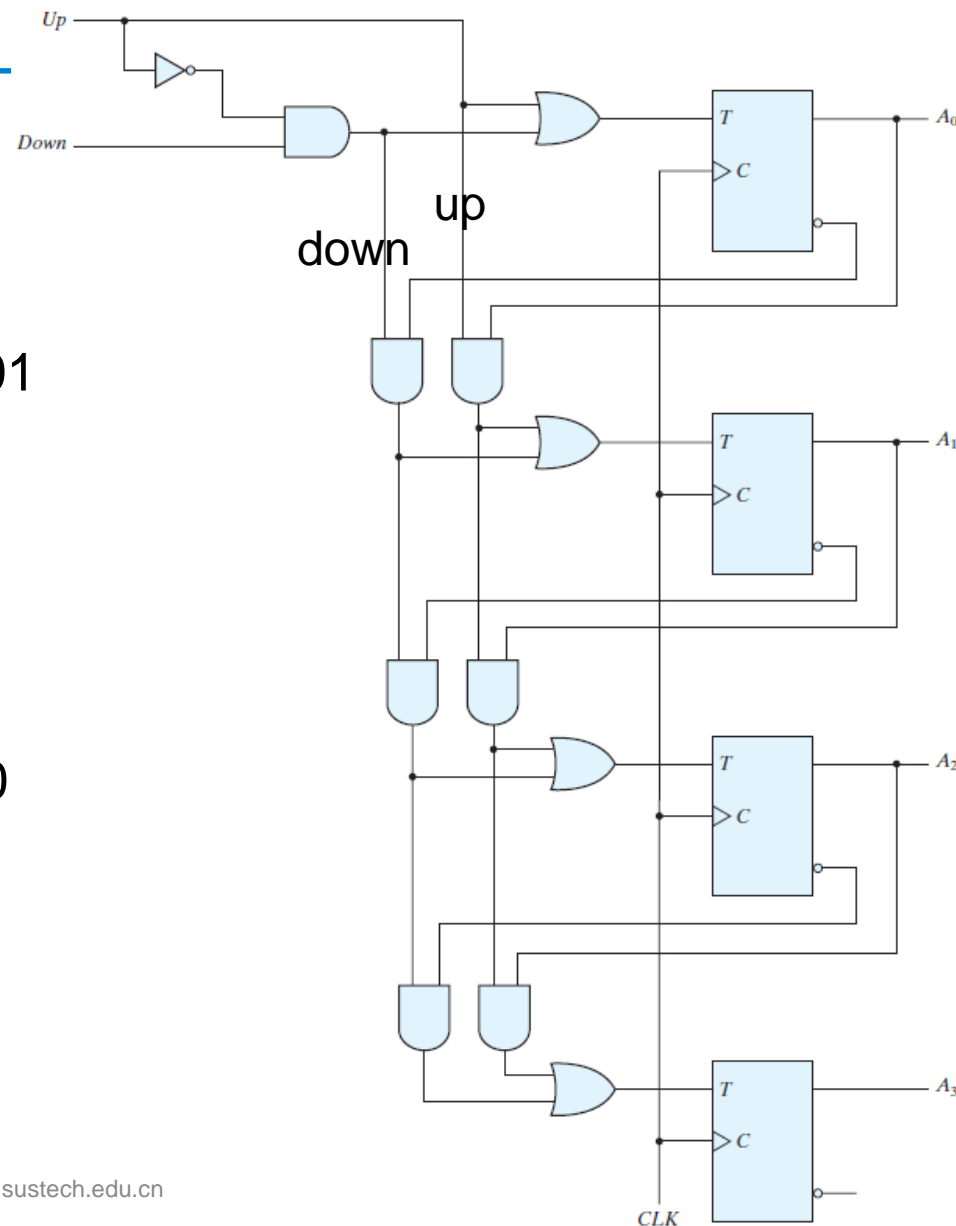- Up=1, Down=0 =>
 - counting up
 - $A_3A_2A_1A_0$
 - $0000 \rightarrow 0001 \rightarrow 0010 \rightarrow 0011 \rightarrow 0100 \rightarrow 0101$
- Up=0, Down=1 =>
 - counting down
 - $A_3A_2A_1A_0$
 - $1111 \rightarrow 1110 \rightarrow 1101 \rightarrow 1100 \rightarrow 1011 \rightarrow 1010$




Shift Register Counters

- Shift registers may be arranged to form different types of counters.
- These shift registers use feedback, where the output of the last flip-flop in the shift register is fed back to the first flip-flop.
- Based on the type of this feedback connection, the shift register counters are classified as
 - ring counter
 - switch-tail ring counter or Johnson counter

Ring Counter

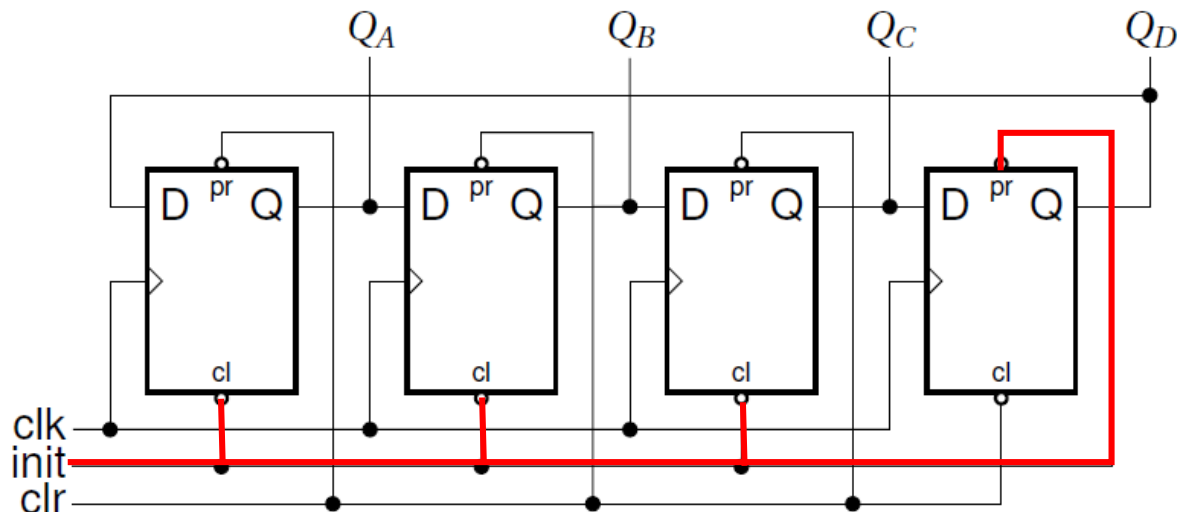- A circular shift register with only one flip-flop being set at any particular time, all others are cleared. (initial value 0001 as in example)
- The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals




1000 → 0100 → 0010 → 0001 →


init	clk	Q_A	Q_B	Q_C	Q_D
L	X	0	0	0	1
H	↑	1	0	0	0
H	↑	0	1	0	0
H	↑	0	0	1	0
H	↑	0	0	0	1

init	clk	Q_A	Q_B	Q_C	Q_D
L	X	0	0	0	1
H	↑	1	0	0	0
H	↑	0	1	0	0
H	↑	0	0	1	0
H	↑	0	0	0	1



Ring Counter for Decoder

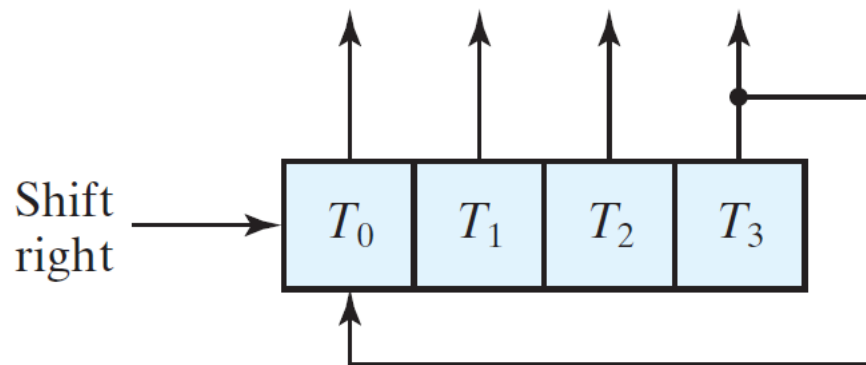

Ring-counter (initial value = 1000)

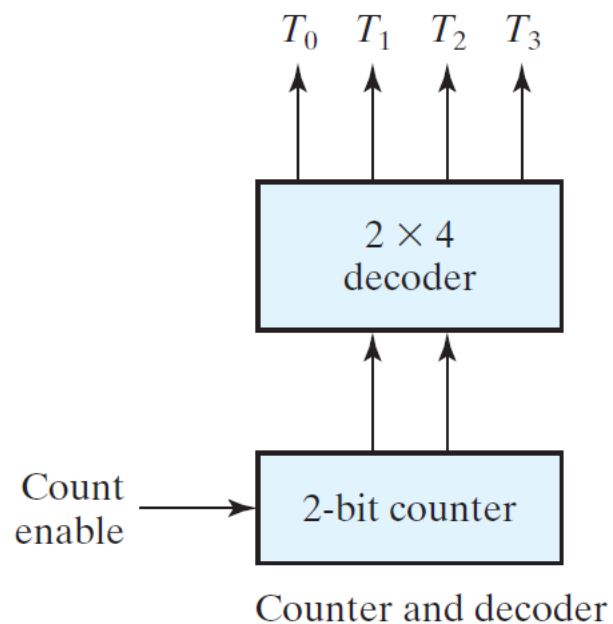



baiyh@sustech.edu.cn

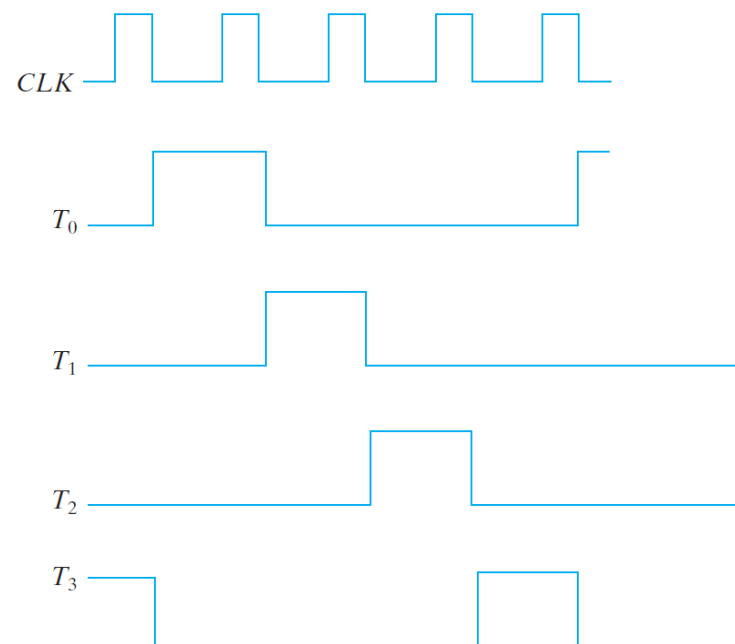 

Sequence of four timing signals

Johnson counter

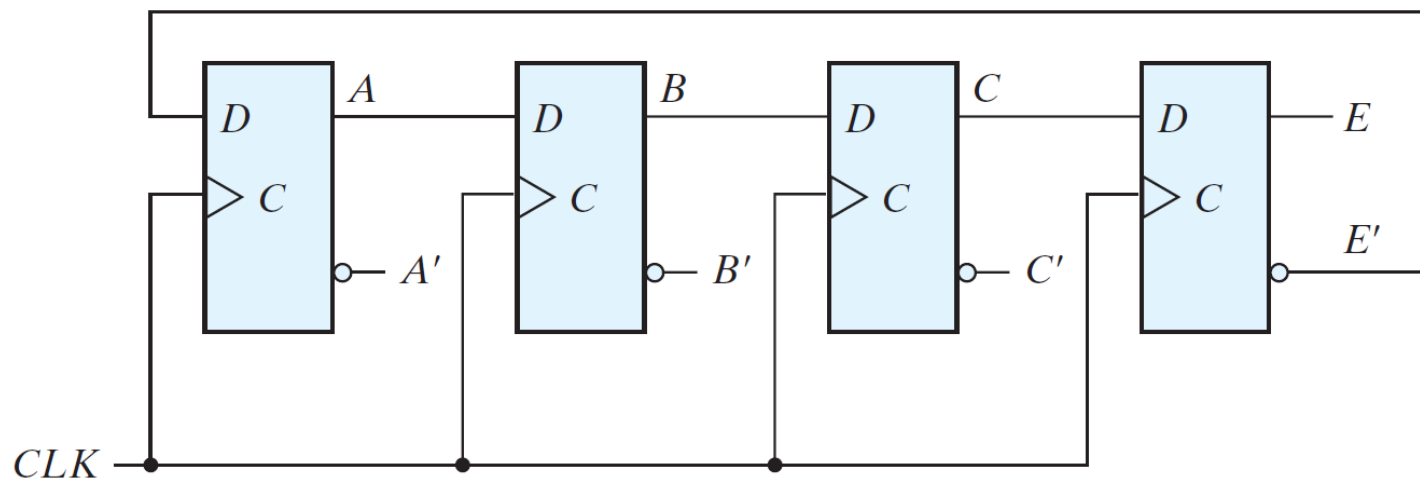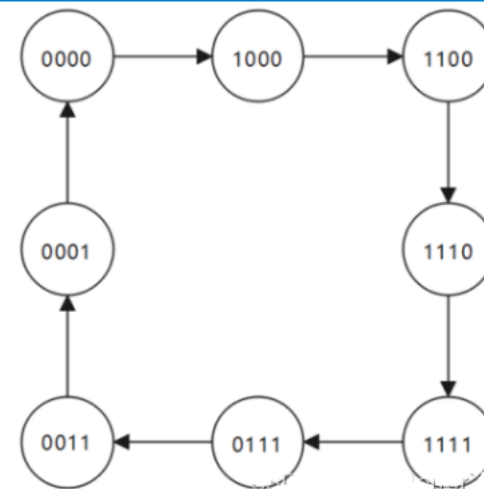
- Switch-tail ring counter: a circular shift register with its complement output of the last flip-flop connected to the input of the first flip-flop
- Johnson counter is a k-bit switch-tail ring counter will go through a sequence of $2k$ distinguishable states (initial value 0000 as in example)



Sequence number	Flip-flop outputs			
	A	B	C	E
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1

Johnson counter for decoder

- Using AND gates for one-hot outputs

 

AND gate required
for output

$A'E'$
 AB'
 BC'
 CE'
 AE
 $A'B$
 $B'C$
 $C'E$

Outline

- Various types of registers
- Sequence generator with shift register
- Asynchronous counter
- Synchronous counter
- **Design a synchronous counter**


Design a Synchronous Counter

Recall: Design Procedure of Sequential Circuits

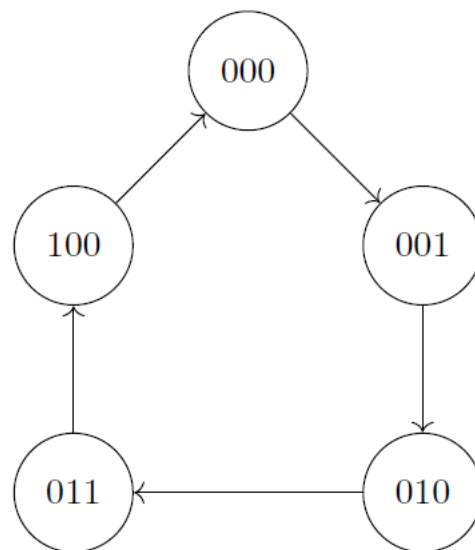1. Specification: design description or timing diagram
2. Formulation: develop state diagram
3. Generate next-state table in form of count sequence
4. Choose type of Flip-Flop
5. Derive simplified excitation equations of FFs
6. Draw logic diagram

Modulo-N Counter

- Counters can be designed to generate any desired sequence of states. A divide-by-N counter (also known as a modulo- N counter)
- e.g. mod-5 counter
 - A counter that goes through the following binary repeated sequence: 0, 1, 2, 3, 4, 0, 1, 2, ...




Counters with Unused States

- n flops $\Rightarrow 2^n$ states
- Unused states
 - States that are not used in specifying the FSM, may be treated as don't-care conditions or may be assigned specific next states
- Self-correcting counters
 - Ensure that when a circuit enter one of its unused states, it eventually goes into one of the valid states after one or more clock pulses so that it can resume normal operation
 - Analyze the circuit to determine the next state from an unused state after it is designed

 Example: Counters with Unused States

- Design a counter that goes through the following binary repeated sequence:
0, 1, 2, 4, 5, 6
 - The unused state is 011 & 111, they are considered as don't care conditions.



Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
0	1	1	X	X	X	X	X	X	X	X	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	X	X	X	X	X	X	X	X	X

Example: Counters with Unused States

$A \backslash BC$	00	01	11	10
0	0	0	x	1
1	x	x	x	x

J_A

$A \backslash BC$	00	01	11	10
0	0	1	x	x
1	0	1	x	x

J_B

$A \backslash BC$	00	01	11	10
0	1	x	x	0
1	1	x	x	0

J_C

$A \backslash BC$	00	01	11	10
0	x	x	x	x
1	0	0	x	1

K_A

$A \backslash BC$	00	01	11	10
0	x	x	x	1
1	x	x	x	1


K_B

$A \backslash BC$	00	01	11	10
0	x	1	x	x
1	x	1	x	x

K_C

- $J_A = B$
- $J_B = C$
- $J_C = B'$

- $K_A = B$
- $K_B = 1$
- $K_C = 1$

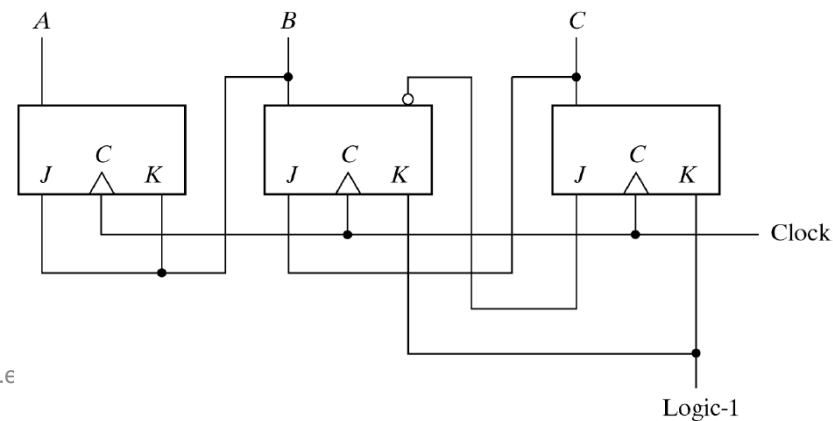

Example: Counters with Unused States

- Unused state & Self-correcting


- What happen if the circuit gets into unused state 011 or 111 because of an error signal?
- Let's analyze the state transition
- $J_A = B$ $K_A = B$
- $J_B = C$ $K_B = 1$
- $J_C = B'$ $K_C = 1$

Present Stat			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	1	1	1	0	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	1	1	0	1

- 100 and 000 are valid state, thus this is a self-correcting counter, it eventually reaches the normal count sequence after one or more clock pulses

 Example: Counters with Unused States


- An alternative design could use additional logic to direct every unused state to a specific next state, to make sure the counter is self-correcting
- To ensure that lock out does not occur, **assuming $111 \rightarrow 000$, $011 \rightarrow 100$** .



Present State			Next State			Flip-Flop Inputs					
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
1	1	1	0	0	0	X	1	X	1	X	1

Lock out problem

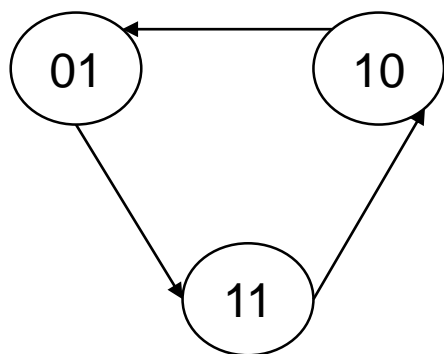- Taking another counter example: It may be possible that the counter might go from one unused state to another and never arrive at a used state.



A(t)	B(t)	A(t+1)	B(t+1)
0	1	1	1
1	1	1	0
1	0	0	1

- $D_A = \sum(1,3), d = \sum(0)$

- $D_B = \sum(1,2), d = \sum(0)$

B	0	1
A		
0	x	1
1	0	1


B	0	1
A		
0	x	1
1	1	0

- $D_A = B, D_B = A \oplus B$

- If state is 00, then next state is still 00 (stuck at 00)

Lock out problem

 - Thus, the solution is to force state 00 transit to another valid state, for example 11




A(t)	B(t)	A(t+1)	B(t+1)
0	1	1	1
1	1	1	0
1	0	0	1
0	0	1	1

- $D_A = ?$, $D_B = ?$

 Exercise: Design a mod-5 Counter

- mod-5 counter

- A counter that goes through the following binary repeated sequence: 0, 1, 2, 3, 4, 0, 1, 2, ...



Present			Next			Flip-flop Inputs					
A_2	A_1	A_0	A_2	A_1	A_0	J_{A2}	K_{A2}	J_{A1}	K_{A1}	J_{A0}	K_{A0}
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	0	0	0	X	1	0	X	0	X

Exercise: Design a mod-5 Counter

A_2	$A_1 A_0$			
	00	01	11	10
0			1	
1	X	X	X	X

$$J_{A2} = A_1 A_0$$

A_2	$A_1 A_0$			
	00	01	11	10
0		1	X	X
1		X	X	X

$$J_{A1} = A_0$$

A_2	$A_1 A_0$			
	00	01	11	10
0	1	X	X	1
1		X	X	X

$$J_{A0} = A_2'$$

A_2	$A_1 A_0$			
	00	01	11	10
0	X	X	X	X
1	1	X	X	X

$$K_{A2} = 1$$

A_2	$A_1 A_0$			
	00	01	11	10
0	X	X	1	
1	X	X	X	X

$$K_{A1} = A_0$$

A_2	$A_1 A_0$			
	00	01	11	10
0	X	1	1	X
1	X	X	X	X

$$K_{A0} = 1$$

Exercise: Design a mod-5 Counter

- Check the unused state, we confirm that all three unused states results in a valid state after one cycle. It is by nature a self-correcting counter.

Present Stat			Next State			Flip-Flop Inputs					
A2	A1	A0	A2	A1	A0	J ₂	K ₂	J ₁	K ₁	J ₀	K ₀
1	0	1	0	1	0	0	1	1	1	0	1
1	1	0	0	1	0	0	1	0	0	0	1
1	1	1	0	0	0	1	1	1	1	0	1

